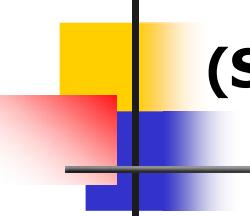


Digital Electronics

(Second Year B. Tech program in Computer Engineering)




Digital Electronics

(Second Year B. Tech program in Computer Engineering)

Unit-II Boolean Algebra and Logic Gates 08 Hrs.

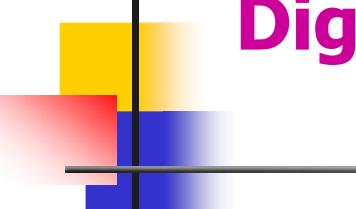
Theorems and Properties of Boolean Algebra, Boolean Functions, Boolean Function Reduction using Boolean Laws, Canonical Forms, Standard SOP and POS Form. Basic Digital Gates: NOT, AND, OR, NAND, NOR, EX-OR, EX-NOR, Positive and Negative Logic, K-Map Method: 2-variable, 3-variable, 4-variable, Don't-Care Conditions, Quine-McCluskey Method, NAND-NOR Realization.



Digital Circuit

A digital circuit is a circuit where the signal must be one of two discrete levels. Each level is interpreted as one of two different states (for example, on/off, 0/1, true/false).


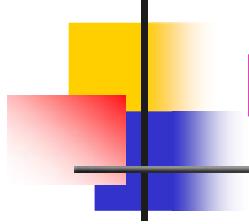
Digital circuits are less susceptible to noise or degradation in quality than analog circuits.



Logic Gates


- Basic Gates – AND, OR and NOT
- Universal Gates – NAND and NOR
- Special Gates – XOR and XNOR

AND Gate IC -7408

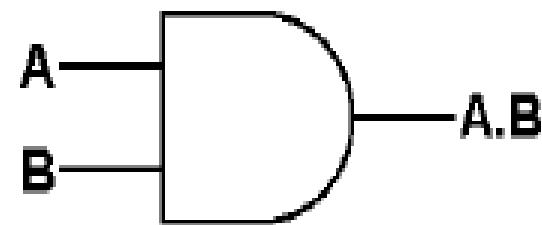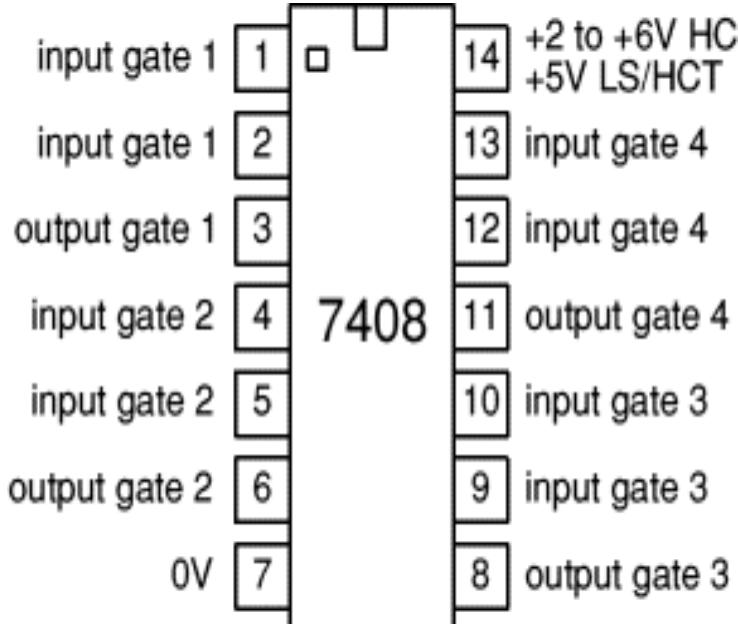



| A | B | $A.B$ |
|-----|-----|-------|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

OR Gate IC -7432

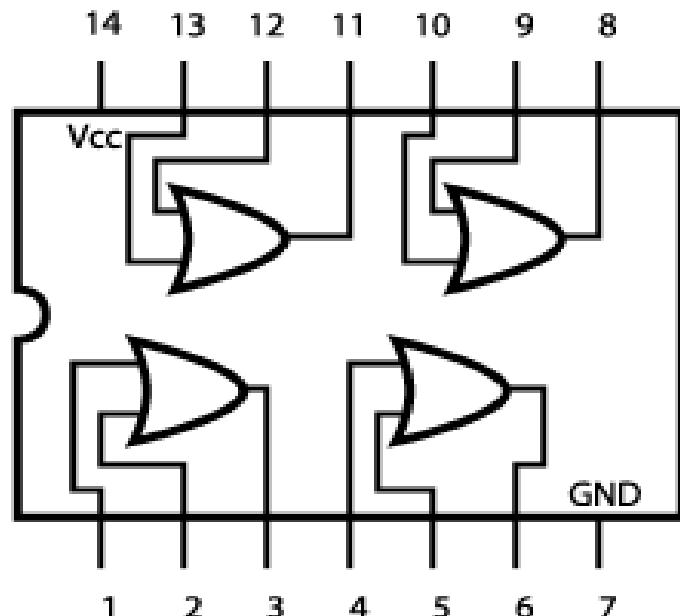



| A | B | $A+B$ |
|-----|-----|-------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 1 |

NOT Gate IC -7404

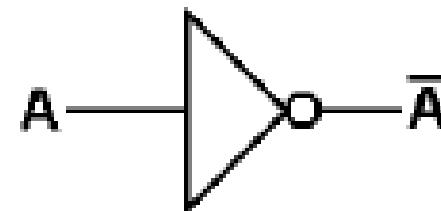
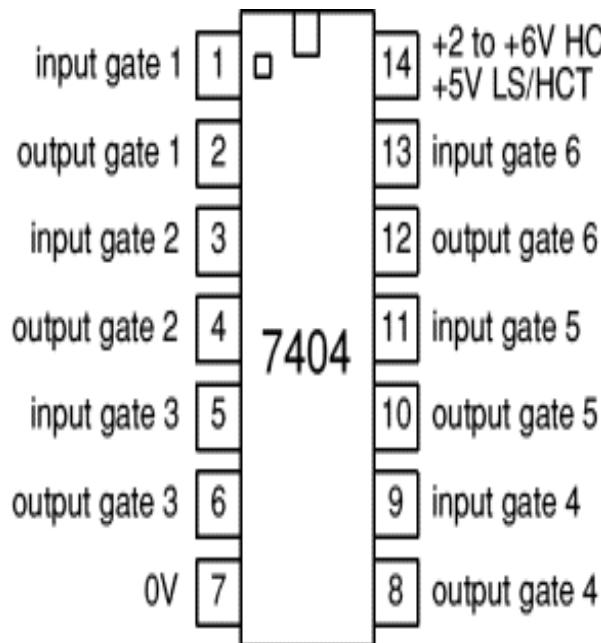


| Input | Output |
|-------|-----------|
| A | \bar{Y} |
| 0 | 1 |
| 1 | 0 |




NAND Gate IC -7400

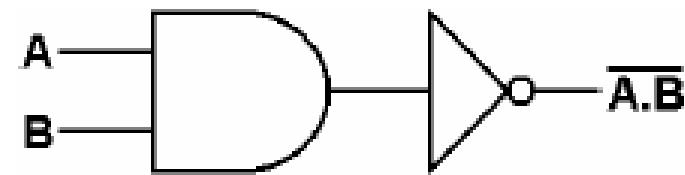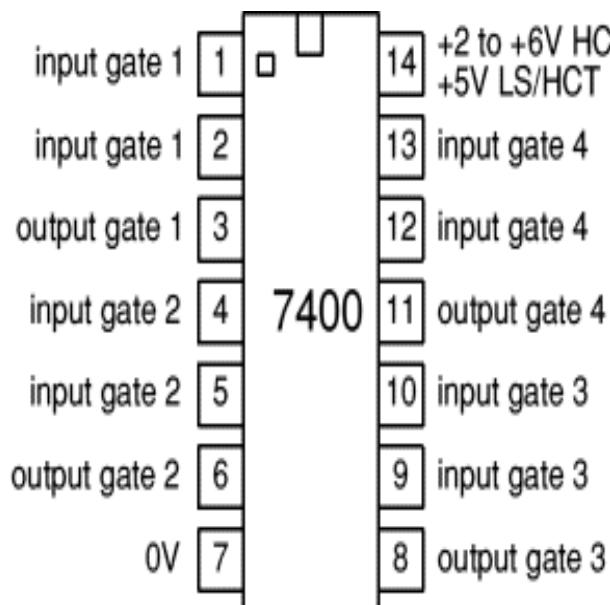

| A | B | $\overline{A \cdot B}$ |
|-----|-----|------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

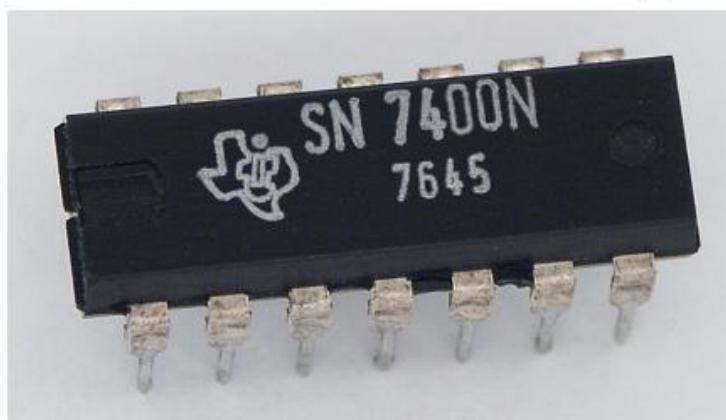
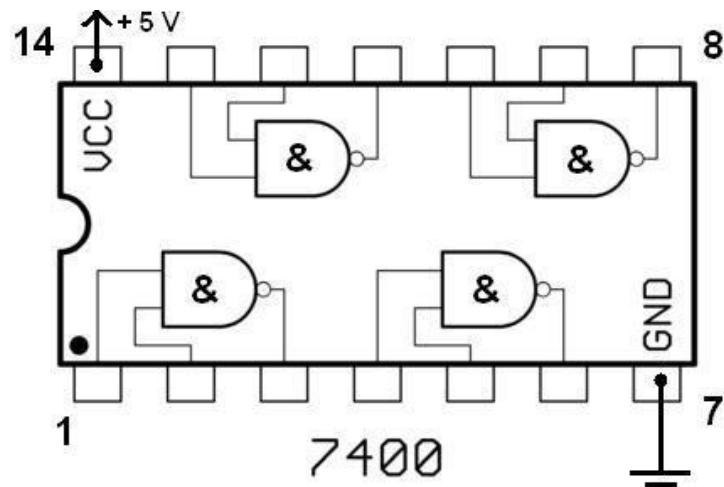


NOR Gate IC -7402

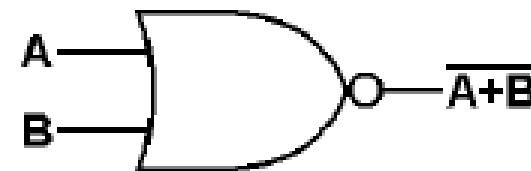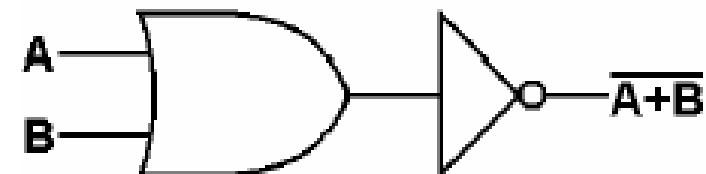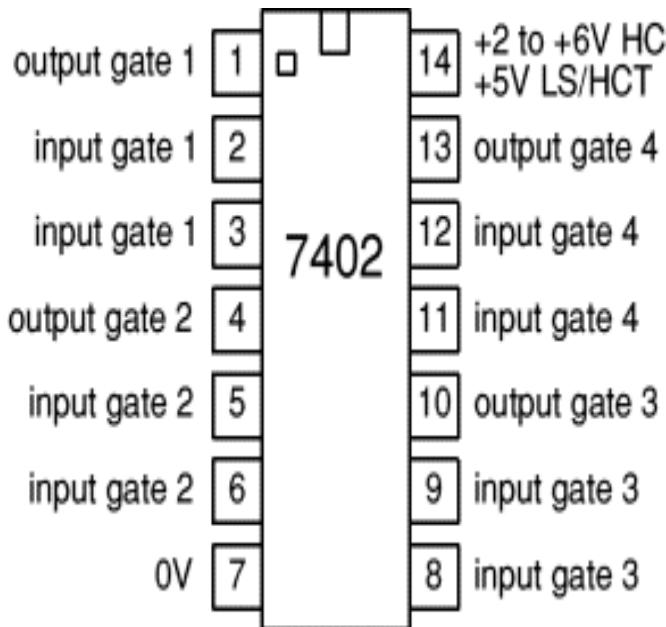

| A | B | $\overline{A+B}$ |
|-----|-----|------------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |


XOR Gate IC -7486

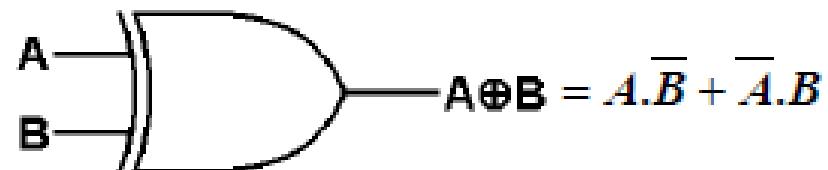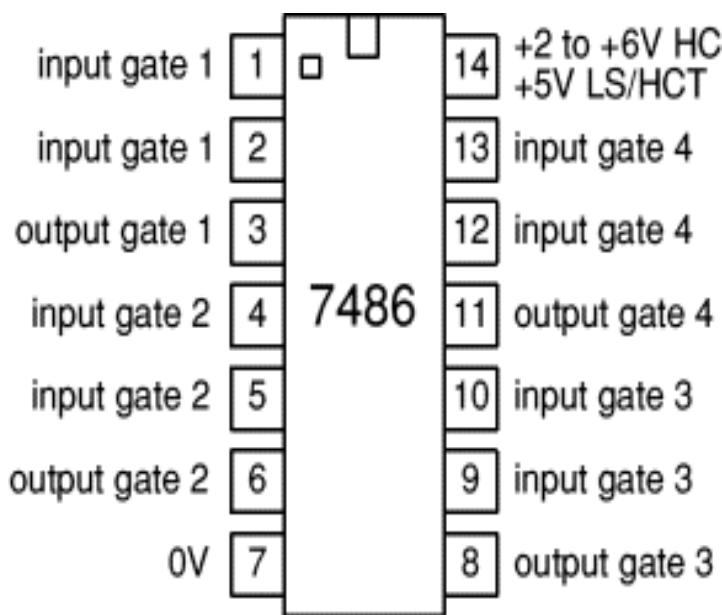

| A | B | $A \oplus B$ |
|-----|-----|--------------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

XNOR


| A | B | $\overline{A \oplus B}$ |
|---|---|-------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

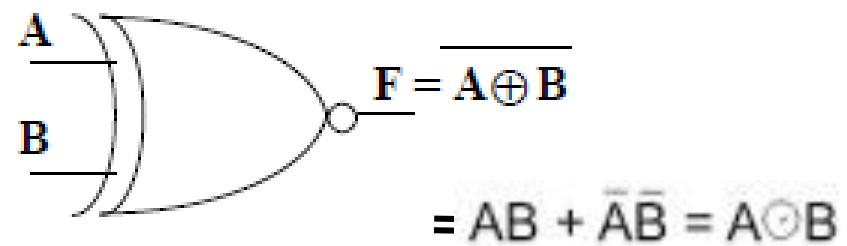


Implementation of Basic Gates using NAND Gate

1) NOT Using NAND


| A | B | $\overline{A \cdot B}$ |
|-----|-----|------------------------|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

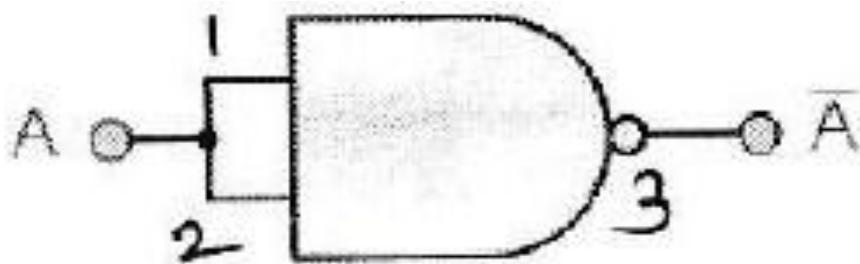


2) AND Using NAND

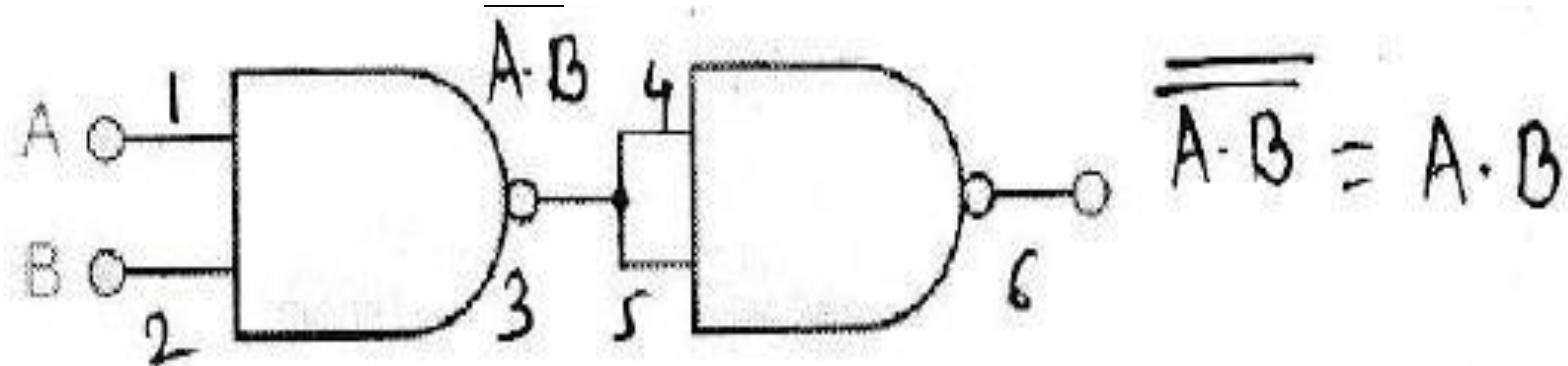

3) OR Using NAND

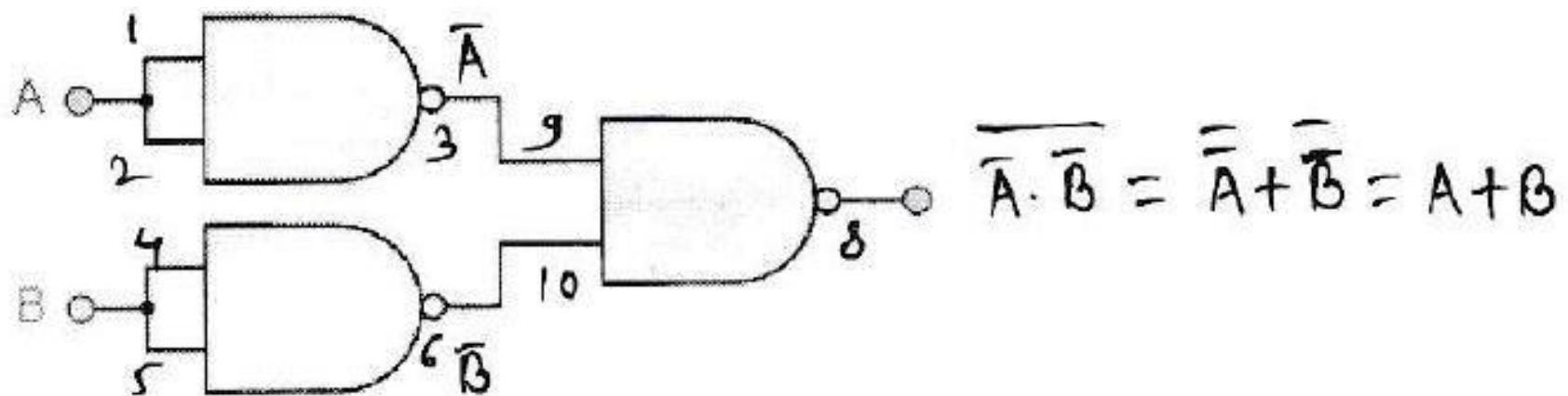

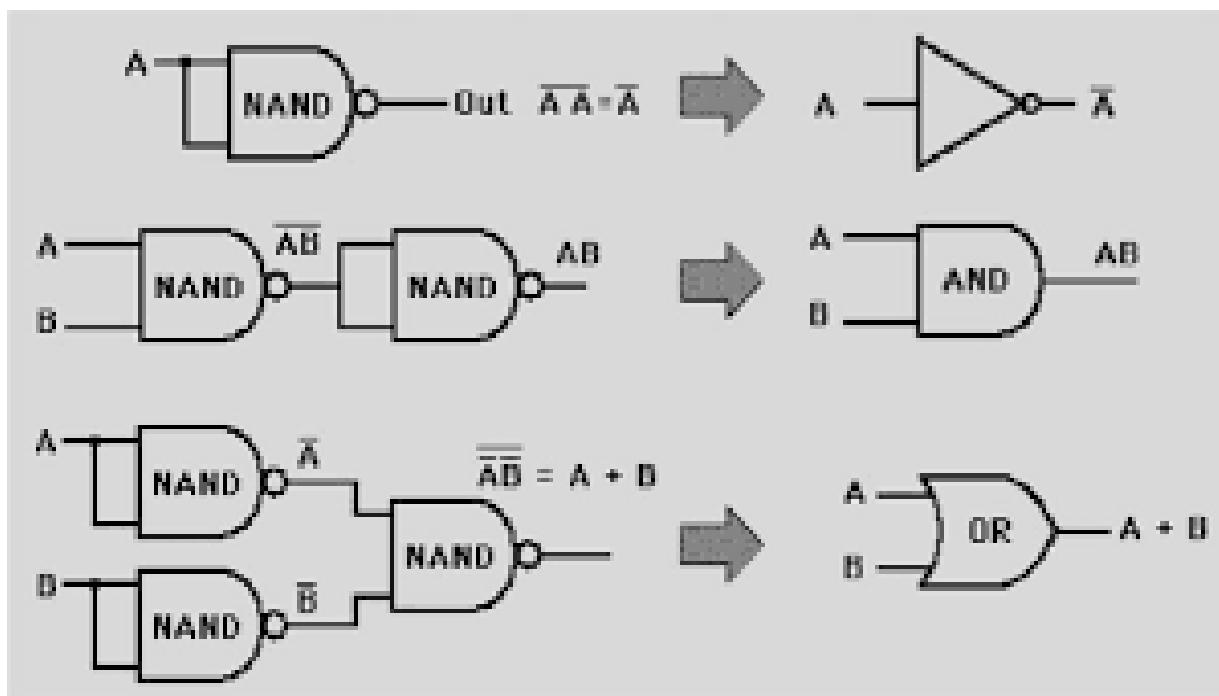
Implementation of Basic Gates using NAND Gate






**Is it possible to implement special
gates using universal gates ?????**

XOR Using NAND

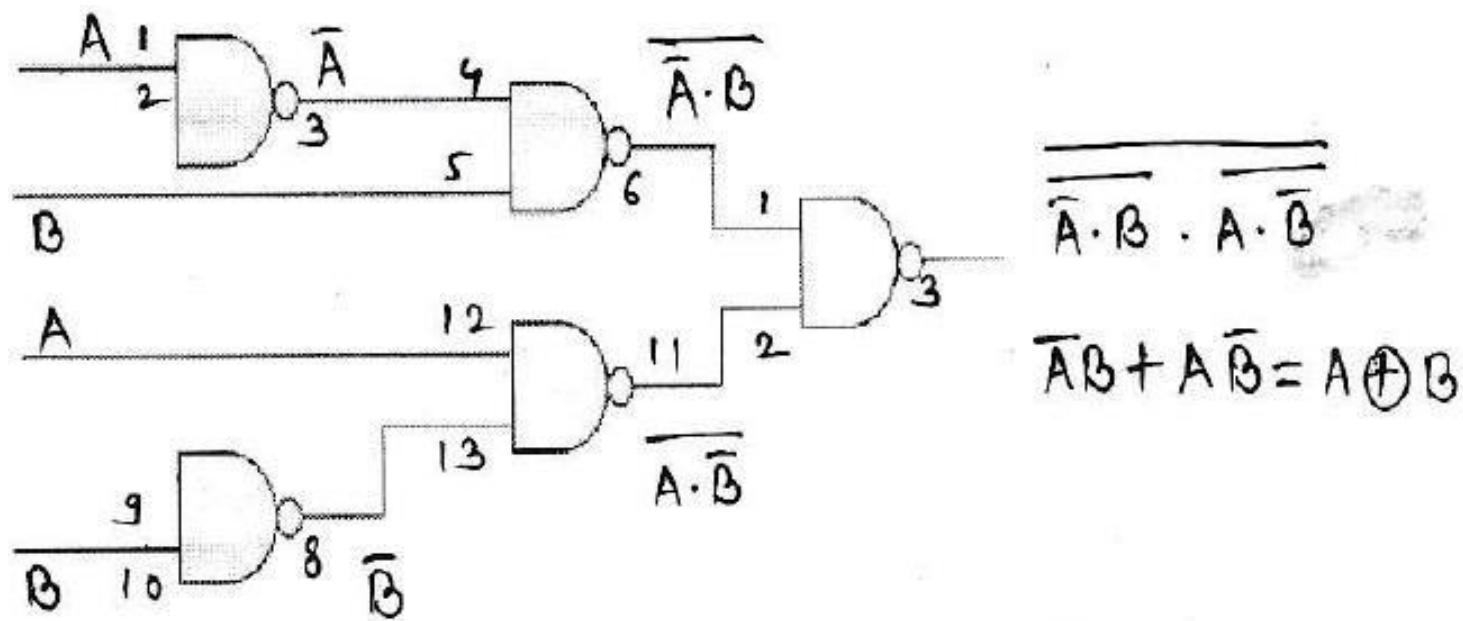


XNOR Using NAND

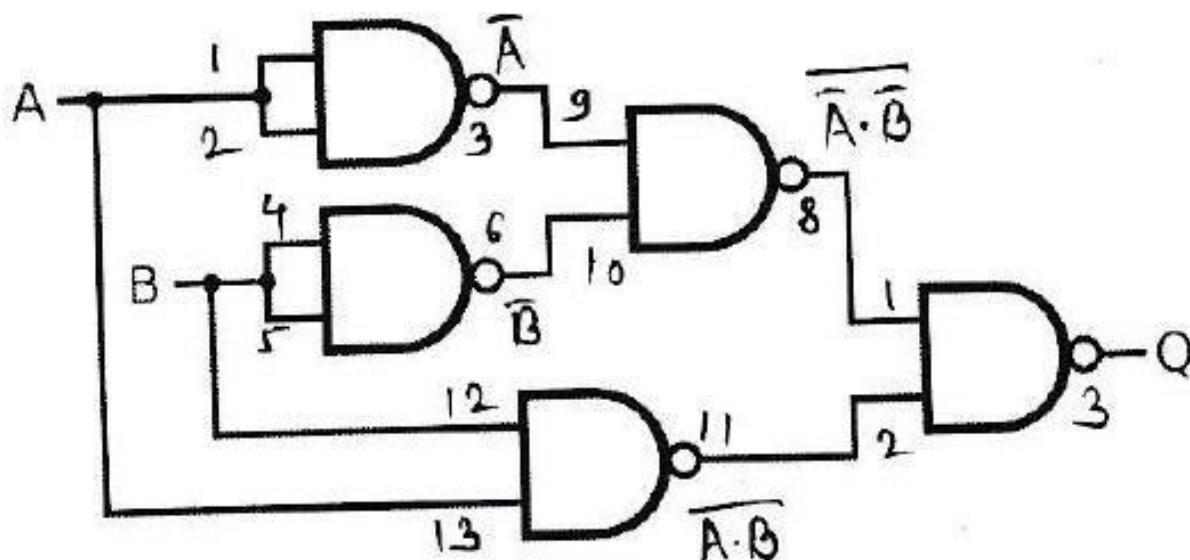

$$\overline{\overline{A} \cdot \overline{B}} \cdot \overline{\overline{A} \cdot B}$$


$$\overline{A} \overline{B} + A \cdot B = A \oplus B$$

NOR Using NAND

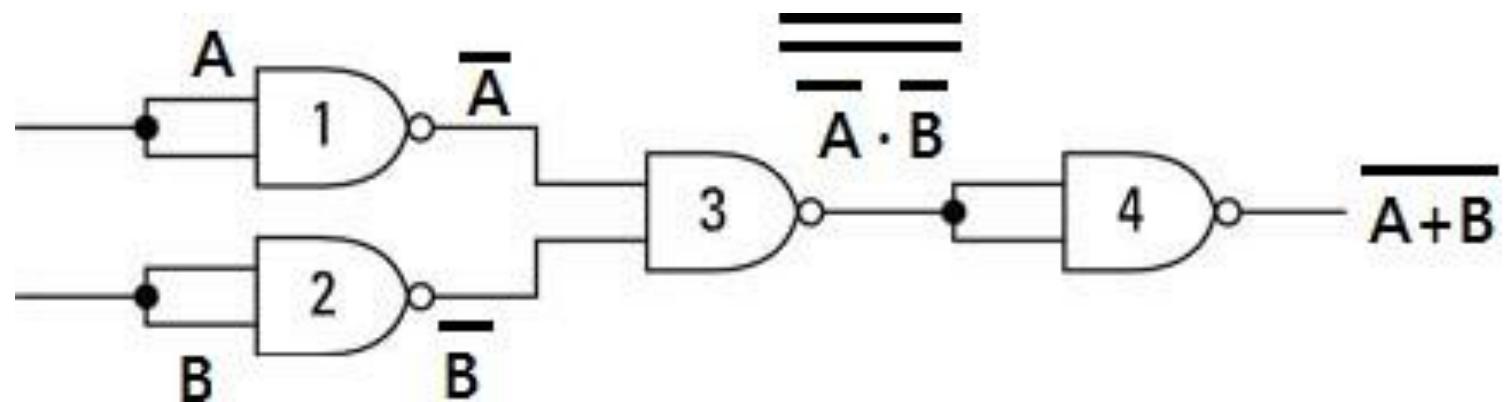


Implementation of Basic Gates using NOR Gate

1) NOT Using NOR

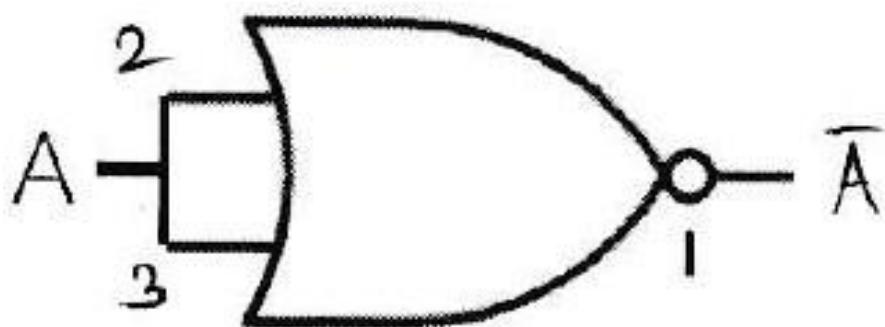


| A | B | $\overline{A + B}$ |
|-----|-----|--------------------|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |


2) AND Using NOR

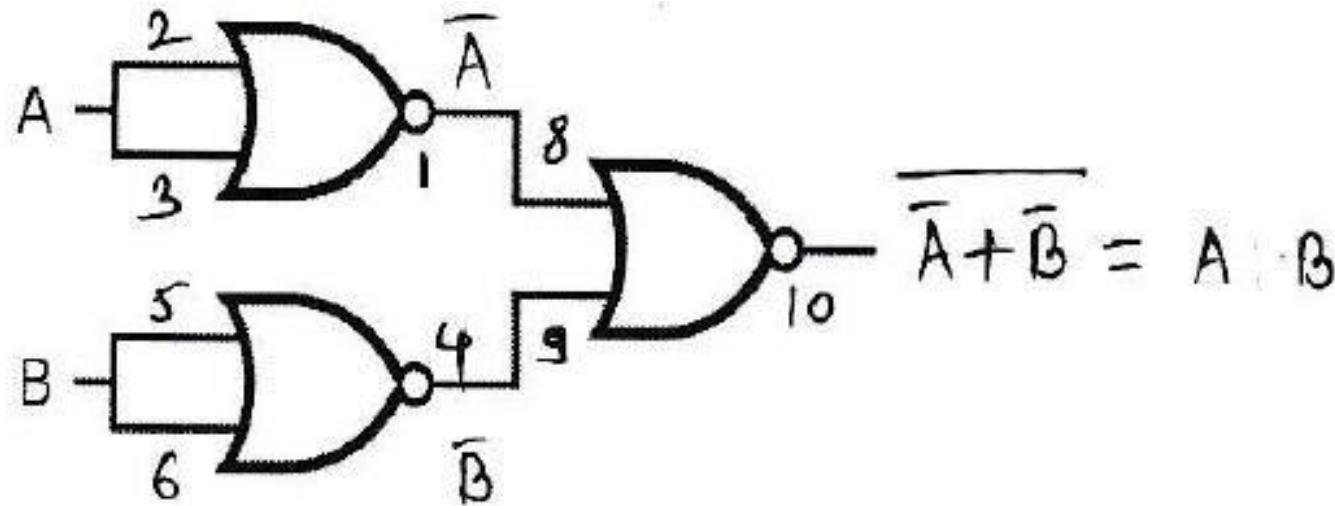


3) OR Using NOR

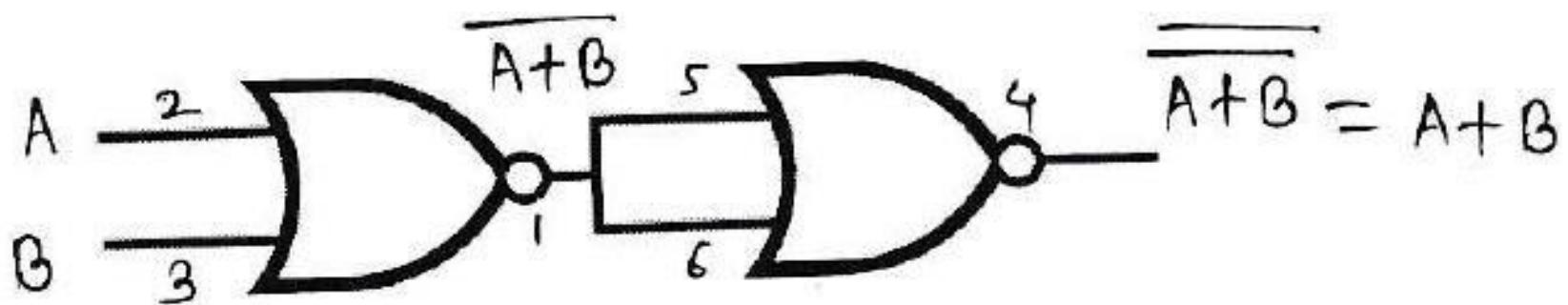


XOR Using NOR

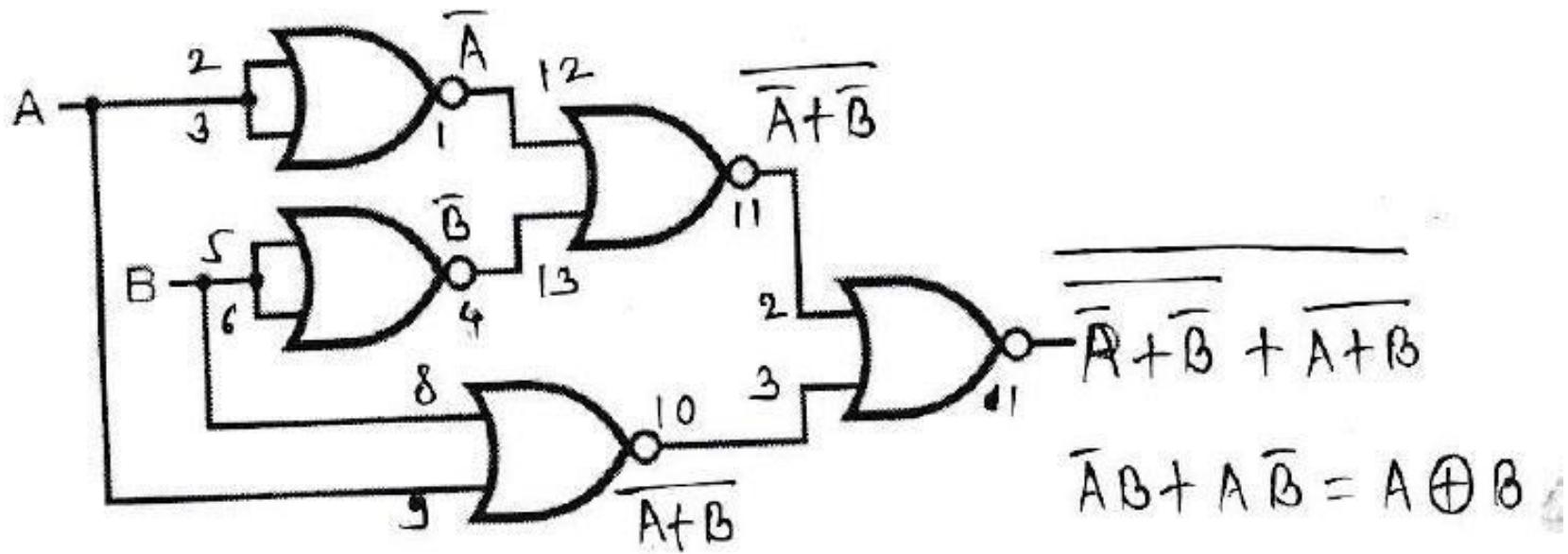

XNOR Using NOR

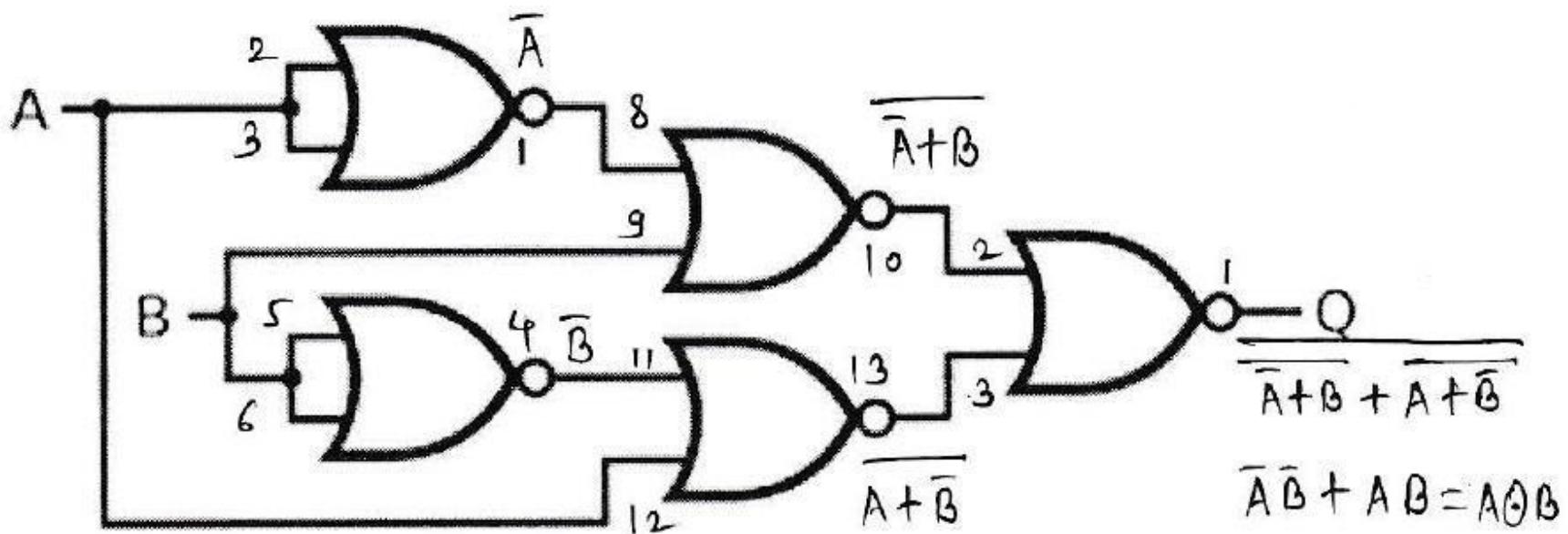

NAND Using NOR

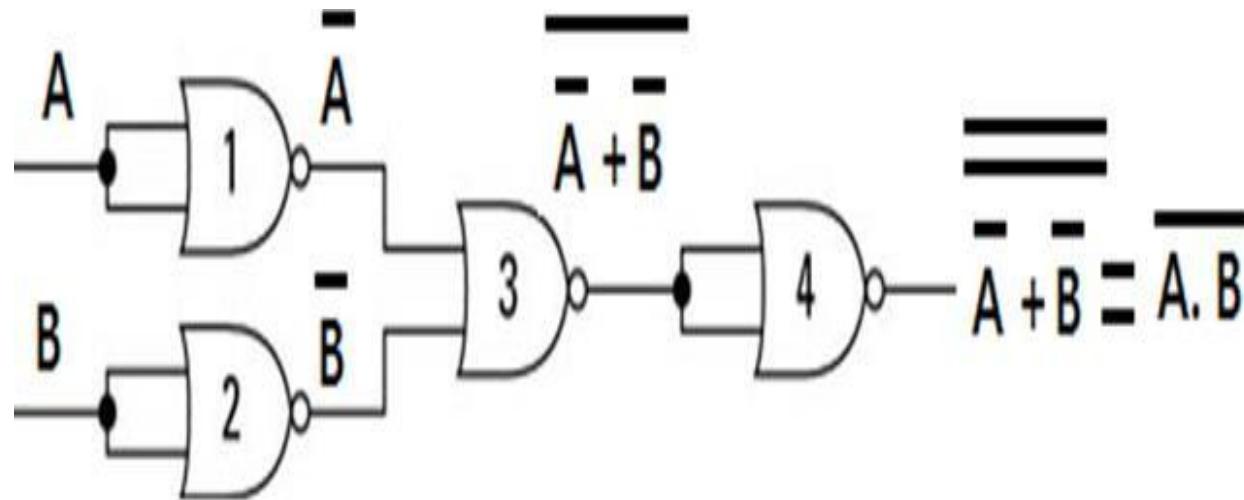

Breadboard Connection


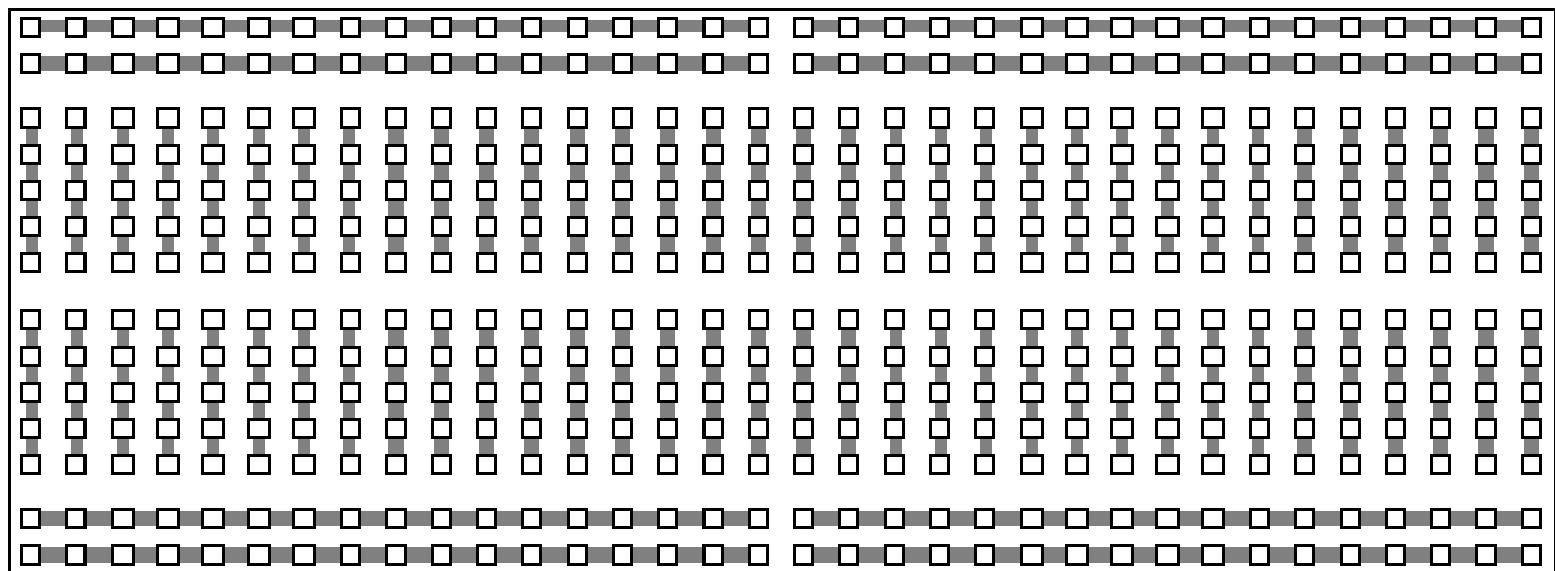


Figure 9: Connection pattern used in the breadboard

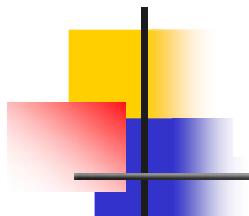


LED

Anode


+

Cathode

-

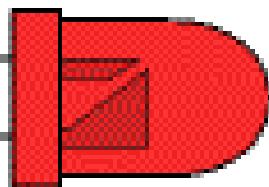


Circuit symbol:

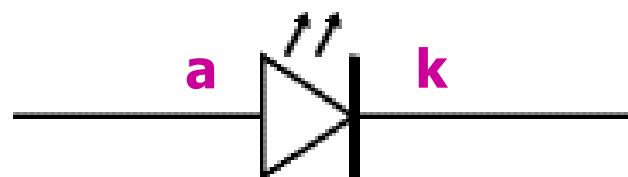


a

k

flat

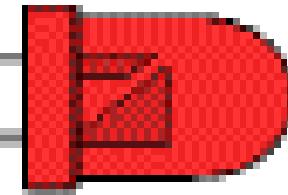

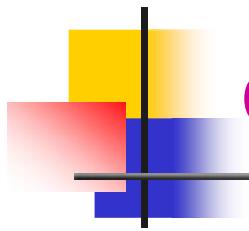
The cathode is the short lead and there may be a slight flat on the body of round LEDs




Colours of LEDs

LEDs are available in red, orange, amber, yellow, green, blue and white.

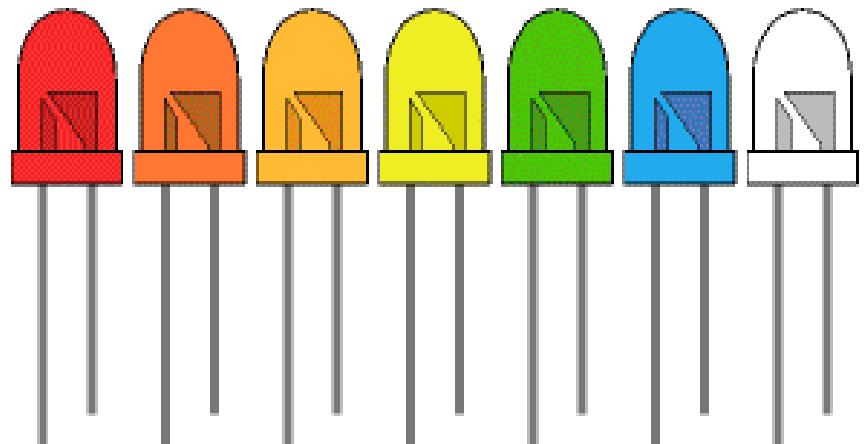Blue and white LEDs are much more expensive than the other colours



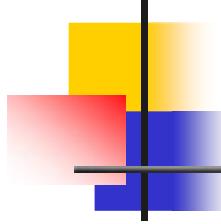The colour of an LED is determined by the semiconductor material, not by the colouring of the 'package' (the plastic body).



Boolean Laws & Theorems

1) AND Laws

$$A \cdot \bar{A} = 0$$

$$A \cdot A = A$$

$$A \cdot 1 = A$$

$$A \cdot 0 = 0$$



2) OR Laws

$$A + A = A$$

$$A + \bar{A} = 1$$

$$A + 0 = A$$

$$A + 1 = 1$$



3) Complement Laws


$$\overline{\overline{A}} = A$$



4) Idempotent Laws

A.A.A.....=A

A+A+A+...=A

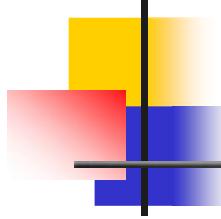

5) Distributive Laws

$$A \cdot (B + C) = A B + A C$$

$$A + BC = (A + B) \cdot (A + C)$$



6) Associative Laws

$$A + (B + C) = (A + B) + C$$

$$A \cdot (B \cdot C) = (A \cdot B) \cdot C$$



7) Commutative Laws

$$\mathbf{A} + \mathbf{B} = \mathbf{B} + \mathbf{A}$$

$$\mathbf{A} \cdot \mathbf{B} = \mathbf{B} \cdot \mathbf{A}$$



8) Other Laws

$$A + \bar{A}B = A + B$$

$$\bar{A} + AB = \bar{A} + B$$

$$A + AB = A$$

$$(A + B)(A + C) = A + BC$$


$$\bar{A} + 1 = 1$$

9) Demorgan's Thm

a) $\overline{A+B} = A \cdot \overline{B}$

Complement of sum is equal to
product of individual
complements


| A | B | $A+B$ | $\overline{A+B}$ | \overline{A} | \overline{B} | $\overline{A} \cdot \overline{B}$ |
|---|---|-------|------------------|----------------|----------------|-----------------------------------|
| 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 |

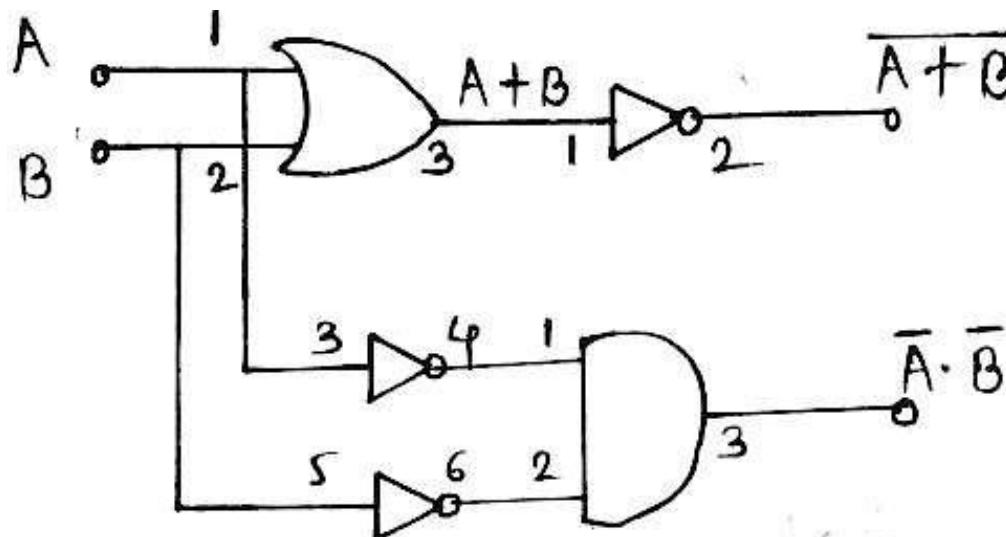


| A | B | $A \cdot B$ | $\overline{A \cdot B}$ | \overline{A} | \overline{B} | $\overline{A} + \overline{B}$ |
|---|---|-------------|------------------------|----------------|----------------|-------------------------------|
| 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 0 | 1 | 0 | 1 | 1 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 0 | 0 |

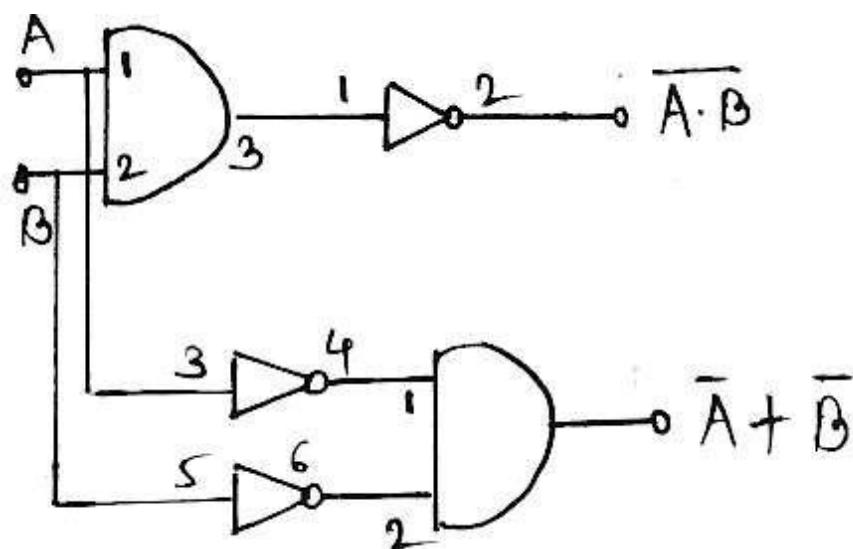b) $\overline{A \cdot B} = \overline{A} + \overline{B}$


Complement of product is equal to sum of individual complements



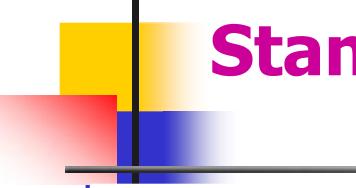

Standard Representation for Logical Functions:

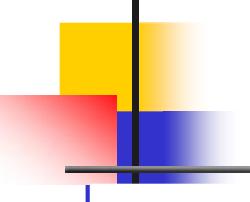
- 1) Literal**
- 2) Sum of Products (SOP)**
- 3) Product of Sums (POS)**
- 4) Standard (Canonical) SOP**
- 5) Standard (Canonical) POS**
- 6) Minterm**
- 7) Maxterm**



Literal

**It is the variable. It may be in the complemented form or
in uncompleted form**

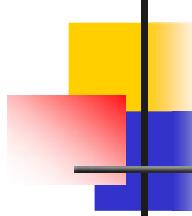For Examples: A , B , \overline{A} , \overline{B} etc




Sum of Products (SOP)

It is an OR (Sum) of AND (Product) terms.

For Example:

$$AB + BC + AC$$

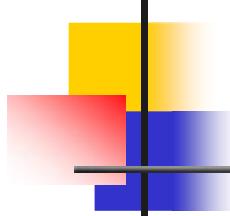


Product of Sum (POS)

It is an AND (Product) of OR (Sum) terms.

For Example:

$$(A+B).(B+C).(A+C)$$

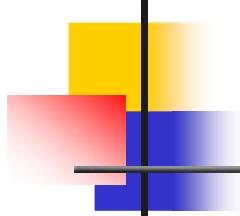

Standard (Canonical) SOP

Conversion of SOP Form into Standard SOP Form

For Example:

$$\text{AB} + \text{BC} + \text{AC}$$

Standard (Canonical) SOP

| | |
|----------------------|-------------------------------|
| 1. $A + 0 = A$ | 7. $A \cdot A = A$ |
| 2. $A + 1 = 1$ | 8. $A \cdot \bar{A} = 0$ |
| 3. $A \cdot 0 = 0$ | 9. $\bar{\bar{A}} = A$ |
| 4. $A \cdot 1 = A$ | 10. $A + AB = A$ |
| 5. $A + A = A$ | 11. $A + \bar{A}B = A + B$ |
| 6. $A + \bar{A} = 1$ | 12. $(A + B)(A + C) = A + BC$ |

A, B, or C can represent a single variable or a combination of variables.

Conversion of SOP Form into Standard SOP Form

For Example:


$$\begin{aligned} & AB + BC + AC \\ & = AB(C+C') + BC(A+A') + AC(B+B') \\ & = ABC + ABC' + ABC + A'BC + ABC + AB'C \\ & = ABC + ABC' + A'BC + AB'C \end{aligned}$$

Given,

$$\begin{aligned} F(A, B, C) &= A + B'C \\ &= A \cdot (B + B')(C + C') + (B'C) \cdot (A + A') \\ &= A \cdot (BC + BC' + B'C + B'C') + AB'C + A'B'C \\ &= ABC + ABC' + AB'C + AB'C' + AB'C + A'B'C \\ &= ABC + ABC' + AB'C + AB'C' + A'B'C \end{aligned}$$

SOP to Canonical SOP

$$\begin{aligned} F &= A\bar{C} + A\bar{B} + BC \quad B + \bar{B} = 1 \\ &= A \cdot (\cancel{B} + \cancel{B}) \cdot \bar{C} + A\bar{B}(\cancel{C} + \cancel{C}) + (\cancel{A} + \cancel{A}) \cdot \bar{C} \cdot \bar{B} \quad A \cdot 1 \cdot \bar{C} = A\bar{C} \\ &= A\bar{C}(B + \bar{B}) + A\bar{B}(\cancel{C} + \bar{C}) + BC(A + \bar{A}) \\ &= A\bar{B}\bar{C} + A\bar{B}\bar{C} + ABC + A\bar{B}C + ABC \end{aligned}$$

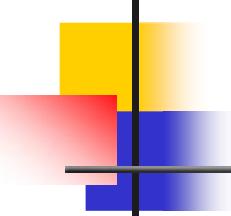

Standard (Canonical) POS


Conversion of POS Form into Standard POS Form.

For Example 1:

$$\begin{aligned}& (A+B).(B+C).(A+C) \\&= (A+B+CC').(AA'+B+C).(A+C+BB') \\&= (\textcolor{red}{A+B+C}).(\textcolor{black}{A+B+C'}).(\textcolor{red}{A+B+C}).(\textcolor{black}{A'+B+C}) .(\textcolor{red}{A+C+B}).(\textcolor{black}{A+C+B'}) \\&= (\textcolor{black}{A+B+C}).(\textcolor{black}{A+B+C'}).(\textcolor{black}{A'+B+C}).(\textcolor{black}{A+C+B'})\end{aligned}$$

For Example 2:
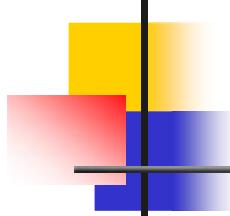
$$\begin{aligned}& (\bar{A} + B + \bar{C})(A + \bar{C}) \\&= (\bar{A} + B + \bar{C})(A + \bar{C} + B\bar{B}) \\&= (\bar{A} + B + \bar{C})(A + \bar{C} + B)(A + \bar{C} + \bar{B}) \\&= (\bar{A} + B + \bar{C})(A + B + \bar{C})(A + \bar{B} + \bar{C})\end{aligned}$$




Minterm

Each individual term in Standard SOP form is called as Minterm.

It is denoted by m or Σ

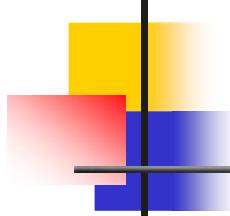In case of Minterms, Complemented variable can be treated as 0's & Uncomplemented variable can be treated as 1's.



Maxterm


Each individual term in Standard POS form is called as Maxterm.

It is denoted by M or Π

In case of Maxterms, Complemented variable can be treated as 1's & Uncomplemented variable can be treated as 0's.

Minterms and Maxterms for Three Variables


| Row No. | A | B | C | Minterms | Maxterms |
|---------|---|---|---|----------------|----------------------|
| 0 | 0 | 0 | 0 | $A'B'C' = m_0$ | $A + B + C = M_0$ |
| 1 | 0 | 0 | 1 | $A'B'C = m_1$ | $A + B + C' = M_1$ |
| 2 | 0 | 1 | 0 | $A'BC' = m_2$ | $A + B' + C = M_2$ |
| 3 | 0 | 1 | 1 | $A'BC = m_3$ | $A + B' + C' = M_3$ |
| 4 | 1 | 0 | 0 | $AB'C' = m_4$ | $A' + B + C = M_4$ |
| 5 | 1 | 0 | 1 | $AB'C = m_5$ | $A' + B + C' = M_5$ |
| 6 | 1 | 1 | 0 | $ABC' = m_6$ | $A' + B' + C = M_6$ |
| 7 | 1 | 1 | 1 | $ABC = m_7$ | $A' + B' + C' = M_7$ |

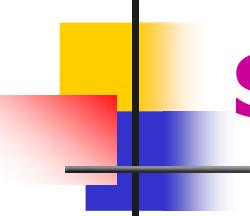

Simplification of Logical Expression


- Algebraic Simplification.
 - Simplify symbolically using theorems/postulates.

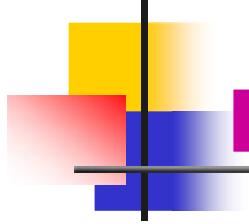- Karnaugh Maps.
 - Diagrammatic technique using 'Venn-like diagram'.



Karnaugh Map (K-Map)



- We have simplified the Boolean functions using Boolean postulates and theorems. It is a time consuming process and we have to re-write the simplified expressions after each step.
- To overcome this difficulty, Karnaugh introduced a method for simplification of Boolean functions in an easy way. This method is known as Karnaugh map method or K-map method.
It is a graphical method, which consists of 2^n cells for 'n' variables. The adjacent cells are differed only in single bit position.

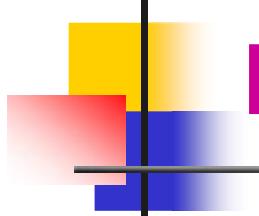

Karnaugh Map (K-Map)

- K-Map for 2 Variable
- K-Map for 3 Variable
- K-Map for 4 Variable
- K-Map for 5 Variable
- K-Map for 6 Variable

K-Map for 2 Variable

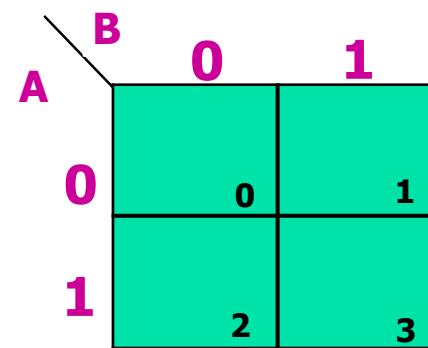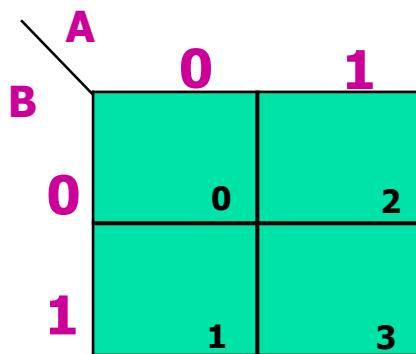

K-Map for 3 Variable

| | | AB | 00 | 01 | 11 | 10 | |
|--|--|----|----|----|----|----|---|
| | | c | 0 | 0 | 2 | 6 | 4 |
| | | 1 | 1 | 3 | 7 | 5 | |


| | | A | 0 | 1 | |
|--|--|----|----|---|---|
| | | BC | 00 | 0 | 4 |
| | | 01 | 1 | 5 | |
| | | 11 | 3 | 7 | |
| | | 10 | 2 | 6 | |

K-Map for 4 Variable

| CD \ AB | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 0 | 4 | 12 | 8 |
| 01 | 1 | 5 | 13 | 9 |
| 11 | 3 | 7 | 15 | 11 |
| 10 | 2 | 6 | 14 | 10 |


| CD \ AB | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00 | 0 | 1 | 3 | 2 |
| 01 | 4 | 5 | 7 | 6 |
| 11 | 12 | 13 | 15 | 14 |
| 10 | 8 | 9 | 10 | 11 |

Binary to Gray Code Conversion


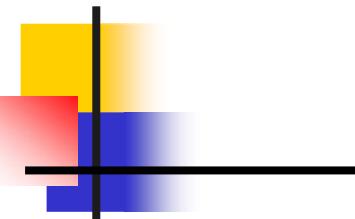


Binary
Code **1 0 0 1**
Gray
Code **1 1 0 1**


| Dec No. | B ₀ | B ₁ | B ₂ | B ₃ | G ₀ | G ₁ | G ₂ | G ₃ | Dec No. |
|---------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|---------|
| 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 |
| 2 | 0 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 3 |
| 3 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 2 |
| 4 | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 6 |
| 5 | 0 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 7 |
| 6 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 5 |
| 7 | 0 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 4 |
| 8 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 12 |
| 9 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 13 |
| 10 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 15 |
| 11 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 14 |
| 12 | 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 | 10 |
| 13 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 11 |
| 14 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 | 9 |
| 15 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 8 |

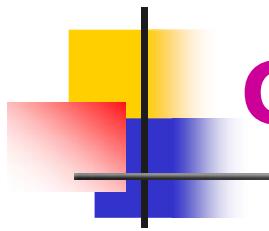



Grouping in 2 Variable K-map

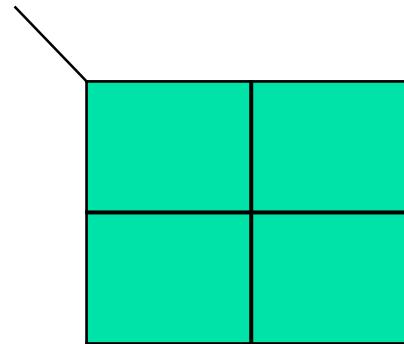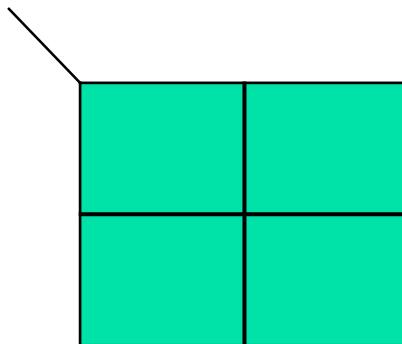

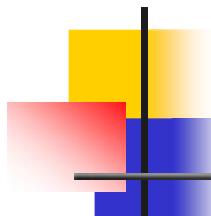- **Quad**
- **Pair**
- **Pair with Fold back**
- **Single**




Grouping in 3 Variable K-map

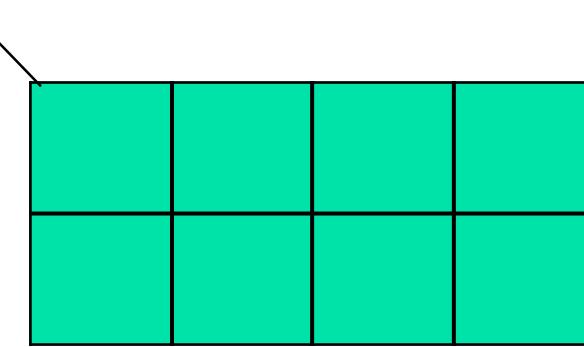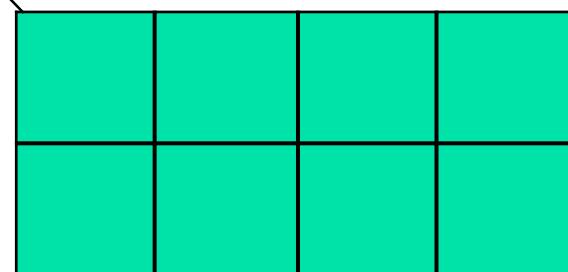



- **Octet**
- **Quad**
- **Quad with Fold back**
- **Pair**
- **Pair with Fold back**
- **Single**

Grouping in 4 Variable K-map

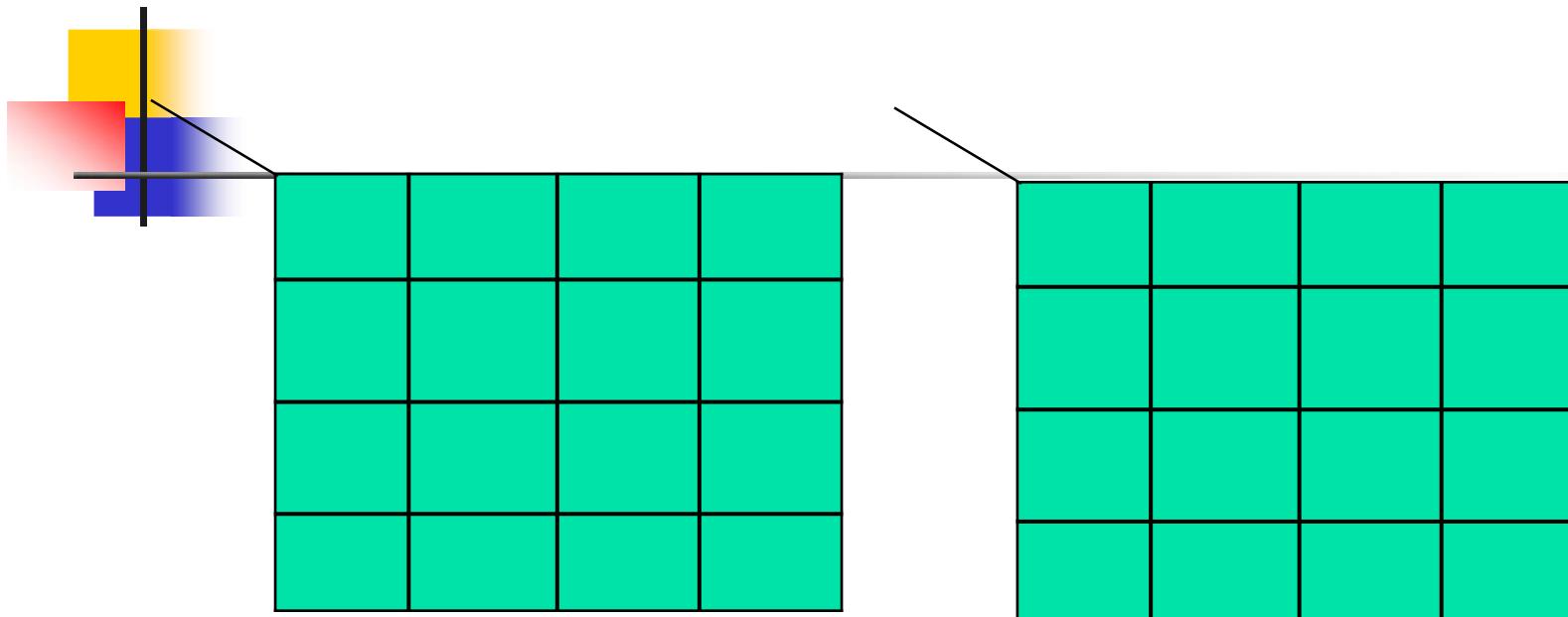

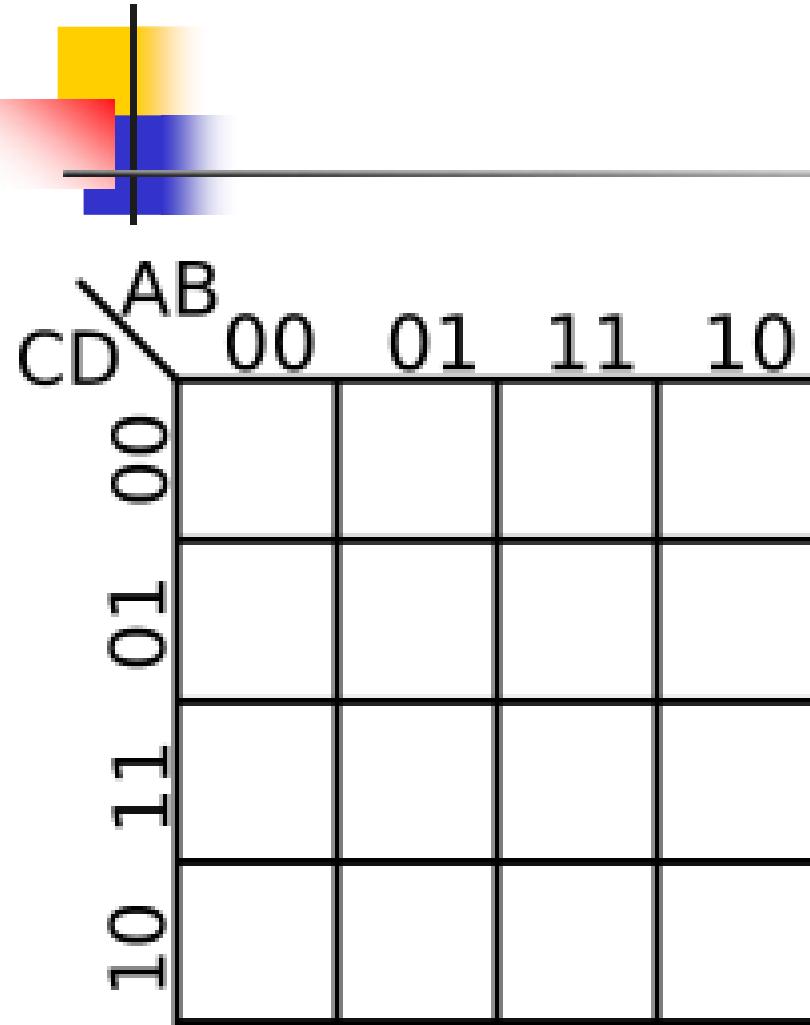- **Hexa**
- **Octet**
- **Octet with Fold back**
- **Quad**
- **Quad with Fold back**
- **Pair**
- **Pair with Fold back**
- **Single**



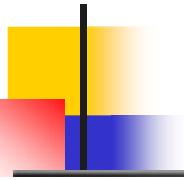

| | | AB | $\bar{A}\bar{B}$ | $\bar{A}B$ | AB | $A\bar{B}$ |
|------------------|----|----|------------------|------------|----|------------|
| | | CD | 00 | 01 | 11 | 10 |
| $\bar{C}\bar{D}$ | 00 | 0 | 4 | 12 | 8 | |
| | 01 | 1 | 5 | 13 | 9 | |
| CD | 11 | 3 | 7 | 15 | 11 | |
| | 10 | 2 | 6 | 14 | 10 | |

SOP

A=1

A'=0

| | \overline{AB} | $A+B$ | $\overline{A+B}$ | $\overline{A+B}$ | $\overline{A+B}$ |
|--------------------|-----------------|-------|------------------|------------------|------------------|
| \overline{CD} | 00 | 01 | 11 | 10 | |
| $C + D$ | 00 | 0 | 4 | 12 | 8 |
| $\overline{C + D}$ | 01 | 1 | 5 | 13 | 9 |
| $\overline{C + D}$ | 11 | 3 | 7 | 15 | 11 |
| $\overline{C + D}$ | 10 | 2 | 6 | 14 | 10 |

POS

$A=0$

$A'=1$

K-map for 5 Variable

| | | $A = 0$ | | | | $A = 1$ | | | | | |
|---------|--|---------|---|----|----|---------|----|----|----|----|----|
| | | BC | | 00 | 01 | 11 | 10 | 00 | 01 | 11 | 10 |
| $D \in$ | | 00 | 0 | 4 | 12 | 8 | 16 | 20 | 28 | 24 | |
| 01 | | 01 | 1 | 5 | 13 | 9 | 17 | 21 | 29 | 25 | |
| 11 | | 11 | 3 | 7 | 15 | 11 | 19 | 23 | 31 | 27 | |
| 10 | | 10 | 2 | 6 | 14 | 10 | 18 | 22 | 30 | 26 | |

Fig. 5.38 *A Five-variable K-map*

K-map for 5 Variable

\bar{A}

| | | BC | | | | |
|----|--|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 | |
| DE | | 00 | 0 | 4 | 12 | 8 |
| DE | | 01 | 1 | 5 | 13 | 9 |
| DE | | 11 | 3 | 7 | 15 | 11 |
| DE | | 10 | 2 | 6 | 14 | 10 |

A

| | | BC | | | | |
|----|--|----|----|----|----|----|
| | | 00 | 01 | 11 | 10 | |
| DE | | 00 | 16 | 20 | 28 | 24 |
| DE | | 01 | 17 | 21 | 29 | 25 |
| DE | | 11 | 19 | 23 | 31 | 27 |
| DE | | 10 | 18 | 22 | 30 | 26 |

K-map for 6 Variable


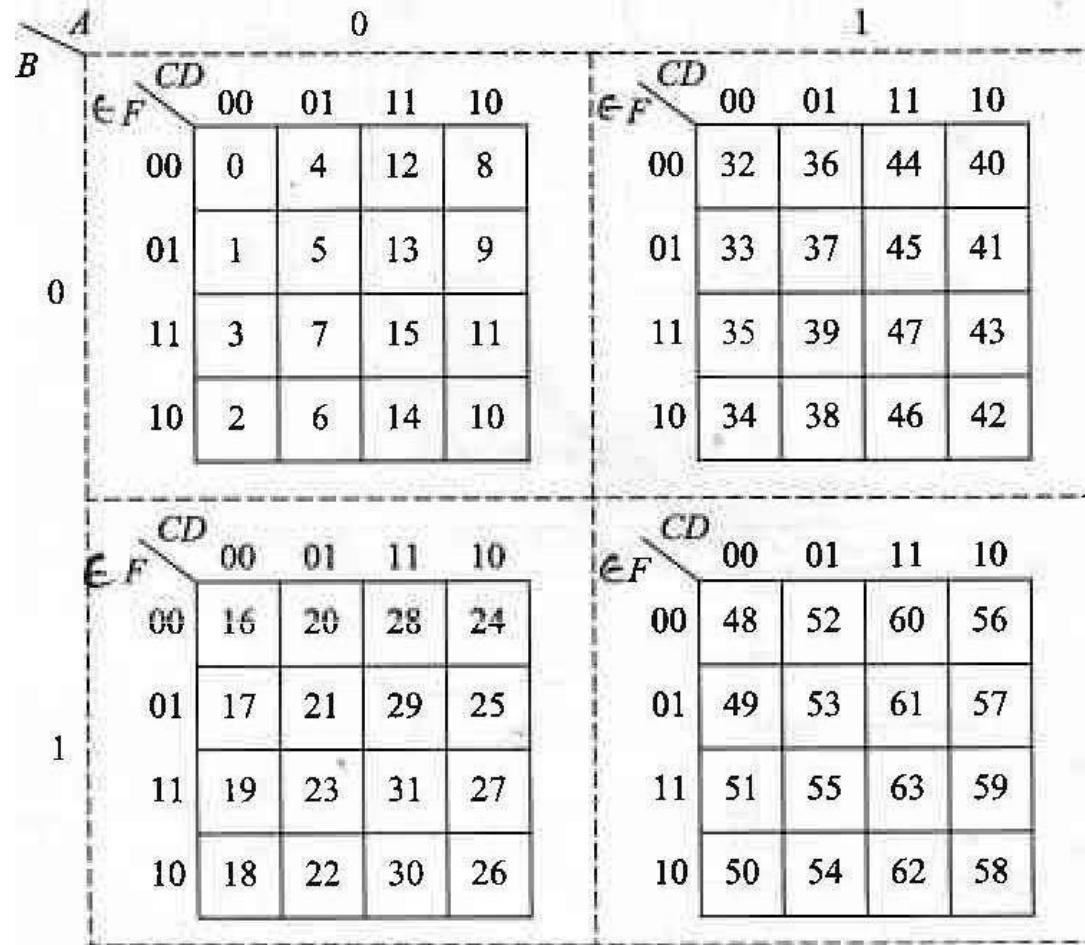


Fig. 5.39 A Six-variable K-map


K-map for 6 Variable

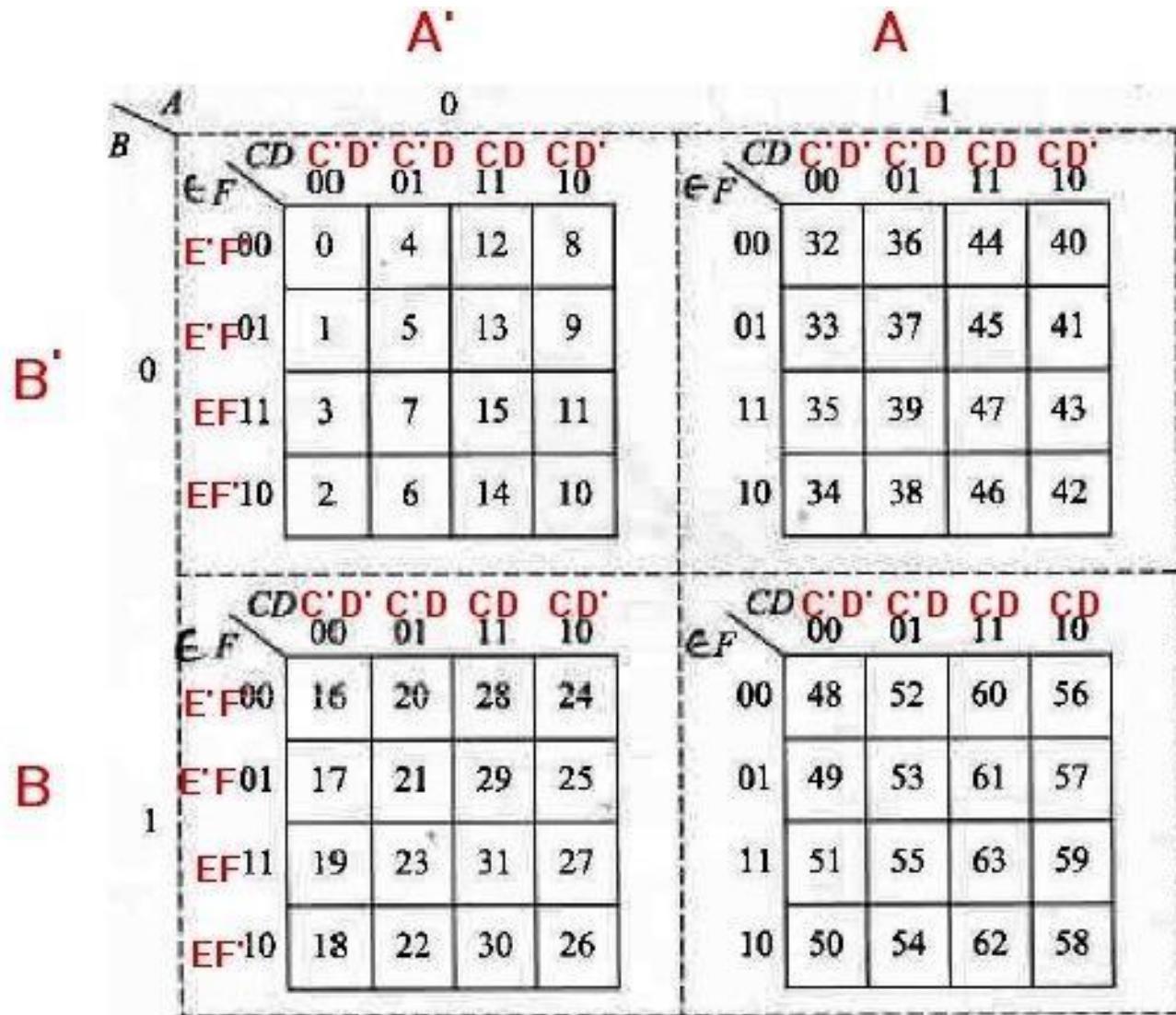

A Six-variable K-map


$$F(A, B, C)$$
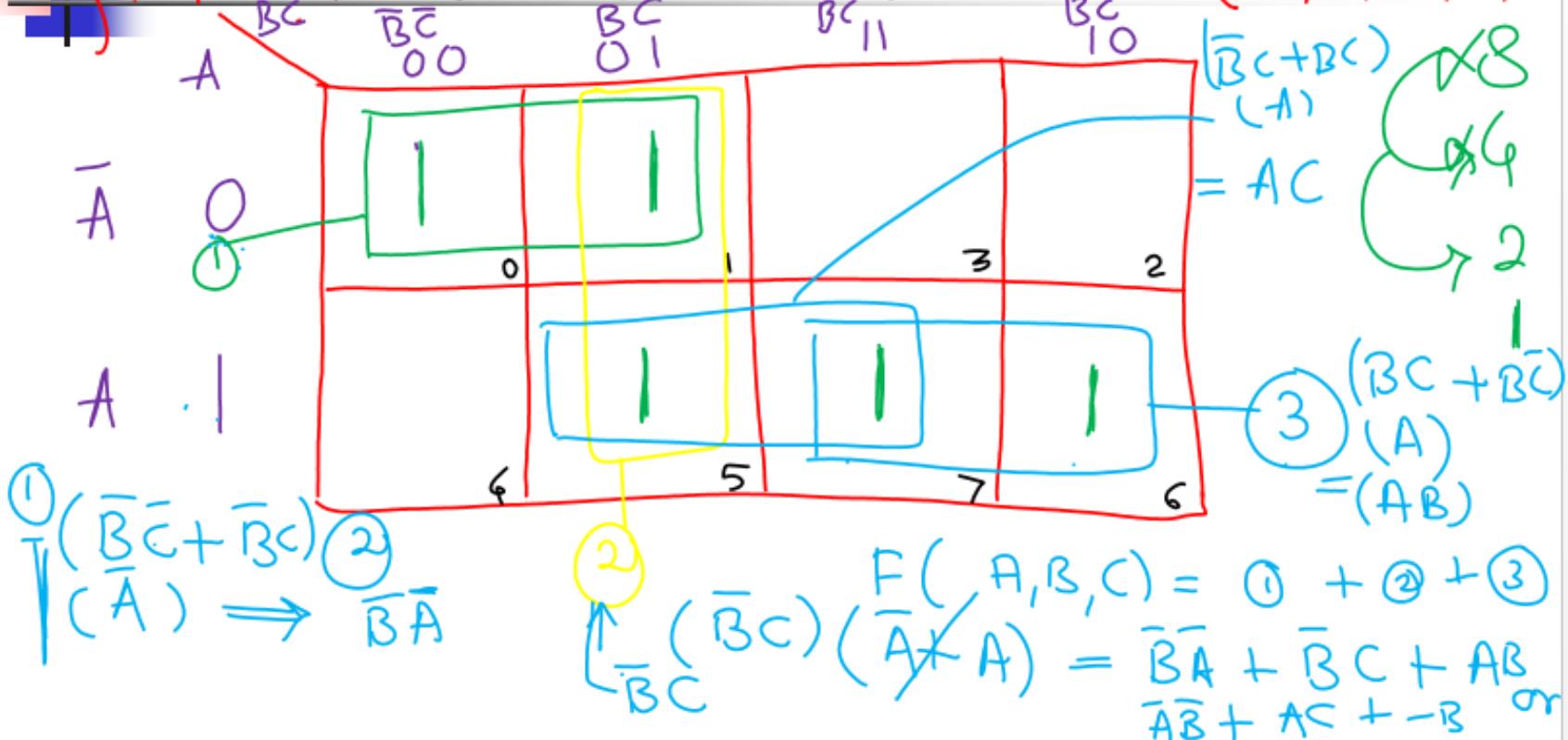
$$\text{Minimize the function} = \sum m(0, 1, 5, 6, 7)$$



$$f(PQ, R, S) = (0, 2, 5, 7, 8, 10, 13, 15)$$
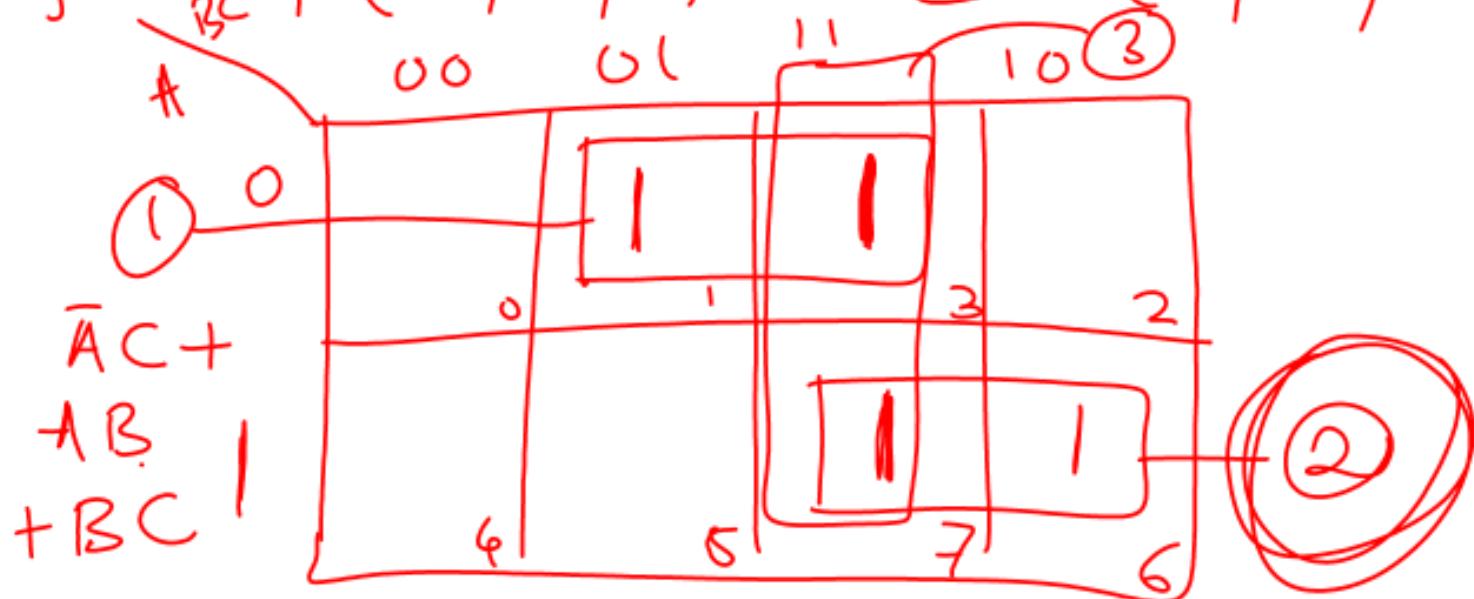
$$\text{Q. } f(A, B, C) = \sum m(1, 3, 6, 7)$$



$$f(P, Q, R, S) = (0, 2, 5, 7, 8, 10, 13, 15) \quad (\bar{R}\bar{S} + R\bar{S}) \\ (\bar{P}\bar{Q} + P\bar{Q})$$

$$PQ \swarrow R \swarrow \quad 00 \quad 01 \quad 11 \quad 10 \quad \textcircled{2} = \bar{S}\bar{Q}$$

| | | | | | | | | | | | | | | | | | | |
|----|----|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|
| | 00 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| 00 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 |
| 01 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 | 0 | 1 |
| 11 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 |
| 10 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 | 0 |

$$(\bar{R}S + RS)(\bar{P}Q + PQ) \\ \textcircled{1} = (SQ)$$

$$\therefore f(P, Q, R, S) \\ = \bar{Q}S + \bar{Q}\bar{S}$$

Q. $F(x, y, z, w) = \sum m(1, 6, 7, 9, 11, 13, 15)$

| xw | 00 | 01 | 11 | 10 | |
|------|----|----|----|----|----|
| yz | 00 | a | 1 | 3 | 2 |
| | 01 | 4 | 5 | 7 | 6 |
| | 11 | 12 | 13 | 15 | 14 |
| | 10 | 8 | 9 | 11 | 10 |

group ① : $\bar{z}w + \bar{z}w \cdot \bar{x}y + \bar{w}x\bar{y}$

group ② : $2x + 2\bar{x} + \bar{y} + \bar{z}\bar{y}$

group ③ : $(\bar{z}w)(\bar{x}\bar{y})$

Ans: $k\bar{x} + 2\bar{x}y + \bar{z}w\bar{x}\bar{y}$


$$f = E(0, 1, 6, 7)$$

$$f = \bar{A}\bar{B} + AB$$

Minimise the four-variable logic function using K-map.


$$f(A, B, C, D) = \Sigma m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14)$$
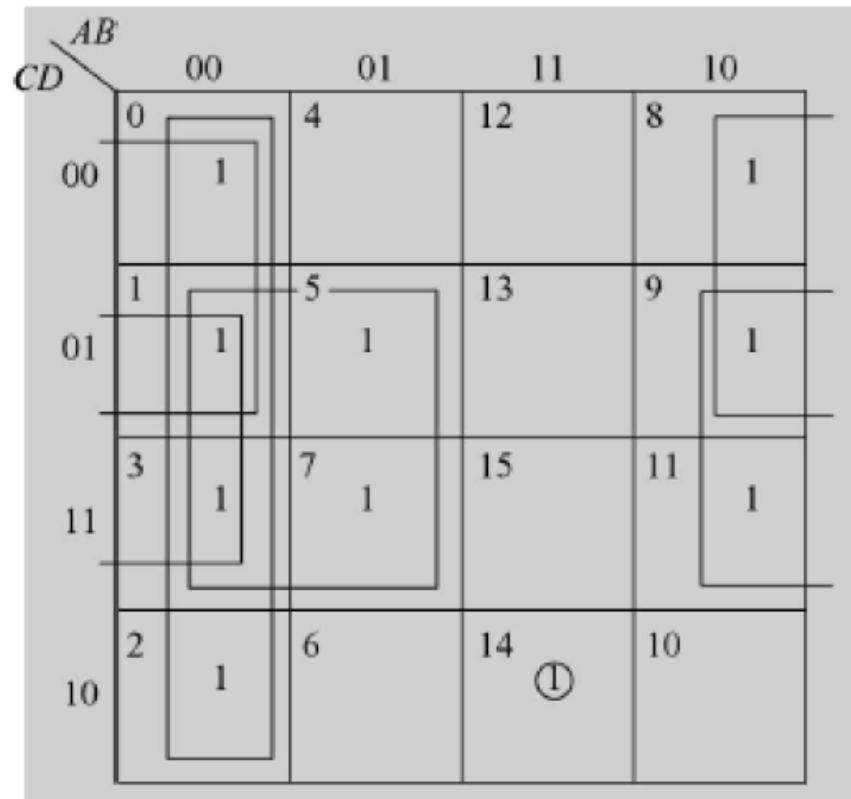
$$f(A, B, C, D) = ABC\bar{D} + \bar{B}\bar{C} + \bar{B}D + \bar{A}D + \bar{A}\bar{B}$$



Determine the minimised expression in SOP form for the truth table given in Table 5.8.

| Inputs | | | | Output |
|--------|---|---|---|--------|
| A | B | C | D | Y |
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

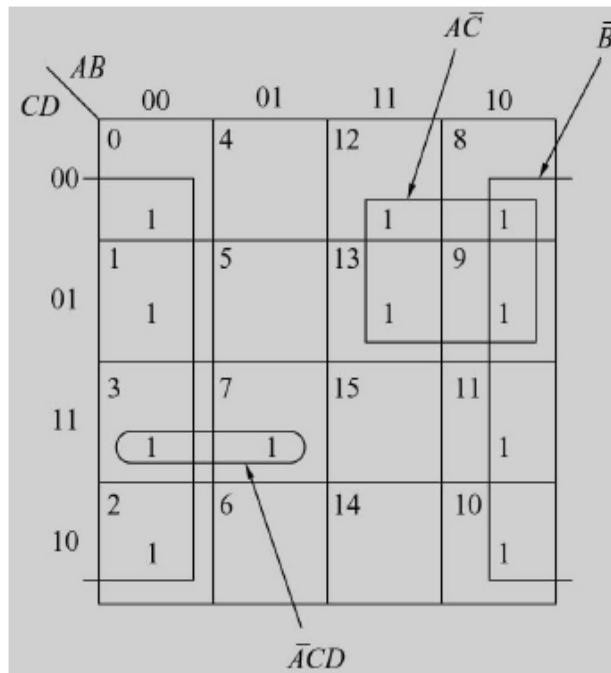

$$Y = \bar{B} + A\bar{C} + \bar{A}CD$$


Minimise the logic function of Eq. (5.23) in POS form

$$f(A, B, C, D) = \sum m(0, 1, 2, 3, 5, 7, 8, 9, 11, 14) \quad (5.23)$$

Solution

Equation (5.23) can be expressed in canonical POS form as

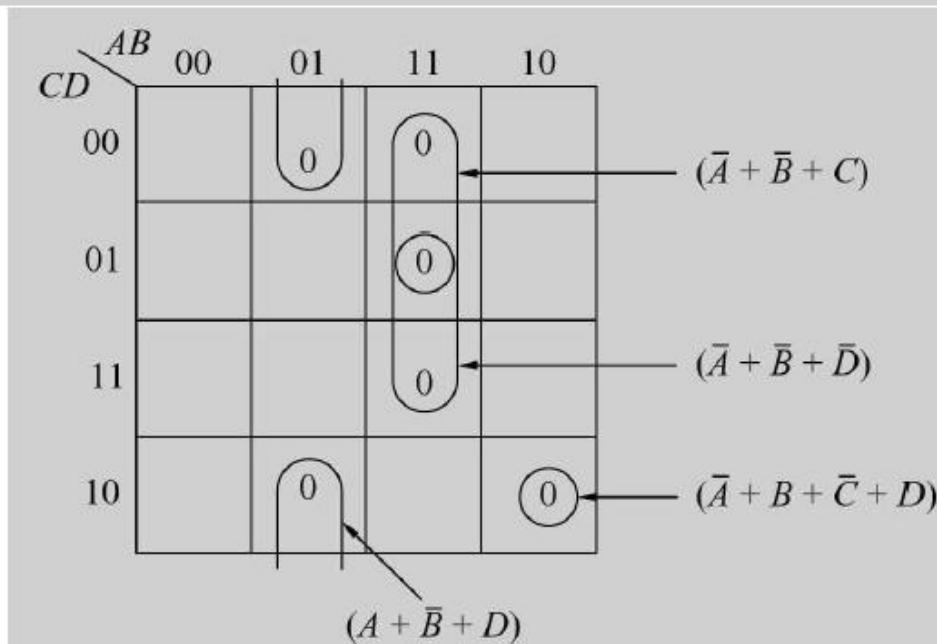
$$f(A, B, C, D) = \prod M(4, 6, 10, 12, 13, 15)$$




$$f = (\bar{A} + B + \bar{C} + D) \cdot (\bar{A} + \bar{B} + C) \cdot (\bar{A} + \bar{B} + \bar{D}) \cdot (A + \bar{B} + D)$$

Minimise the truth table given in Table 5.8 using maxterms.


| Inputs | | | | Output |
|--------|---|---|---|--------|
| A | B | C | D | Y |
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 0 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 0 | 1 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 1 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 0 |

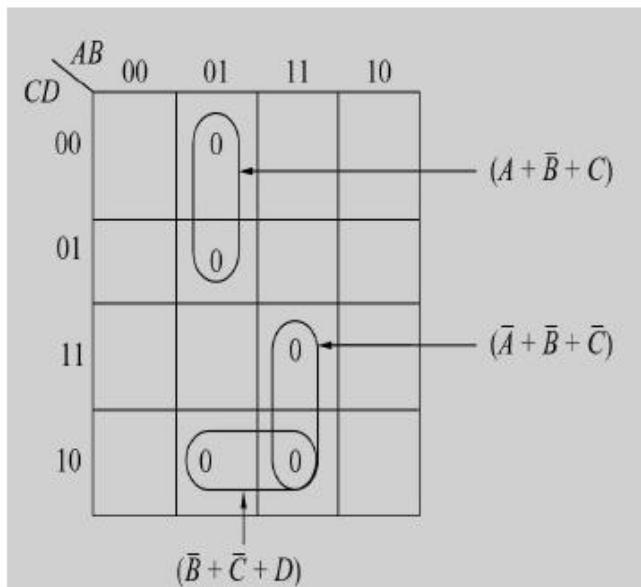

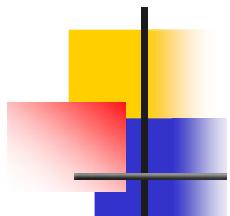
$$Y = (A + \bar{B} + C)(\bar{A} + \bar{B} + \bar{C})(\bar{B} + \bar{C} + D)$$



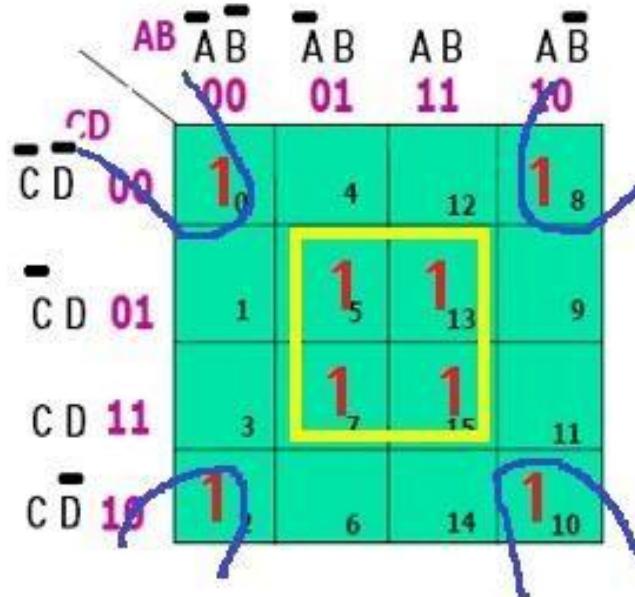
Solve using KMAP $F = m(0,2,5,7,8,10,13,15)$




$$F = BD + B'D'$$

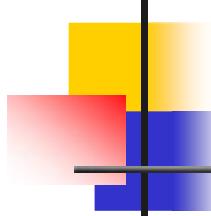

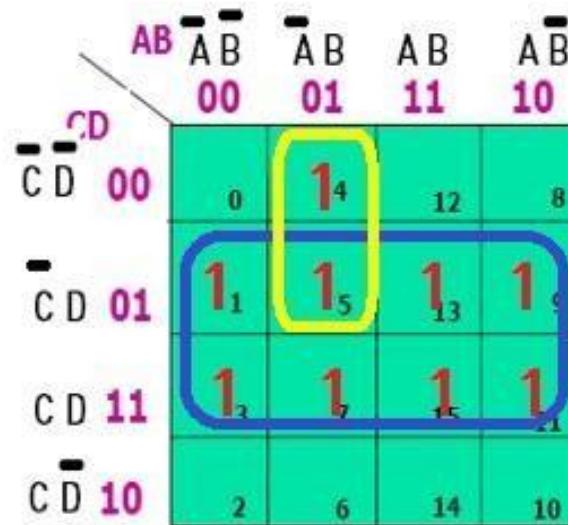
Solve using KMAP $F = m(1, 3, 4, 5, 7, 9, 11, 13, 15)$



$$F = D + A' B C'$$

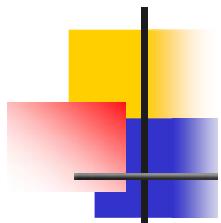

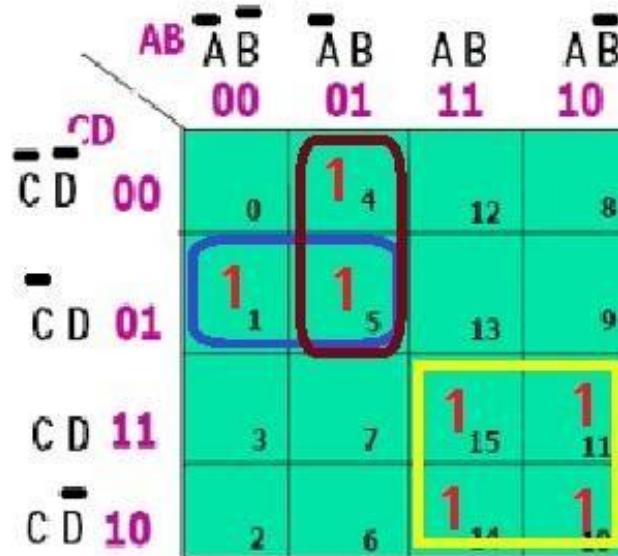Solve using KMAP $F = m(1,4,5,10,11,14,15)$



$$F = AC + A'C'D + A'BC'$$

Minimise the four variable logic function


$$f(A, B, C, D) = AB\bar{C}D + \bar{A}BCD + \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}\bar{D} + A\bar{C} + A\bar{B}C + \bar{B}$$



| | | AB | 00 | 01 | 11 | 10 |
|----|----|----|----|----|----|----|
| | | CD | 00 | 01 | 11 | 10 |
| 00 | 00 | 1 | | 1 | 1 | |
| | 01 | 1 | | 1 | 1 | |
| | 11 | 1 | 1 | | | 1 |
| | 10 | 1 | | | | 1 |



Minimise the four variable logic function

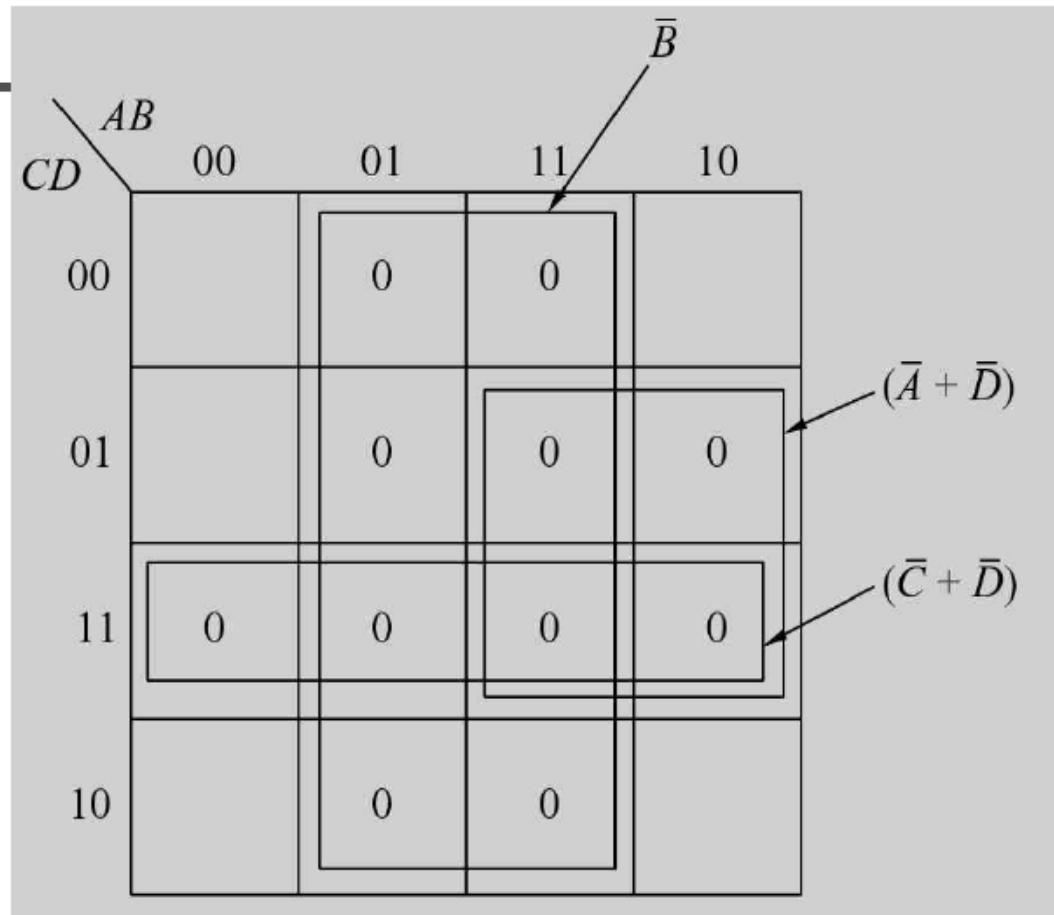
$$f(A, B, C, D) = (A + B + \bar{C} + \bar{D}) \cdot (\bar{A} + C + \bar{D}) \cdot (\bar{A} + B + \bar{C} + \bar{D}) \cdot \\ (\bar{B} + C) \cdot (\bar{B} + \bar{C}) \cdot (A + \bar{B}) \cdot (\bar{B} + \bar{D})$$



$$f(A, B, C, D) = \bar{B} \cdot (\bar{A} + \bar{D})(\bar{C} + \bar{D})$$

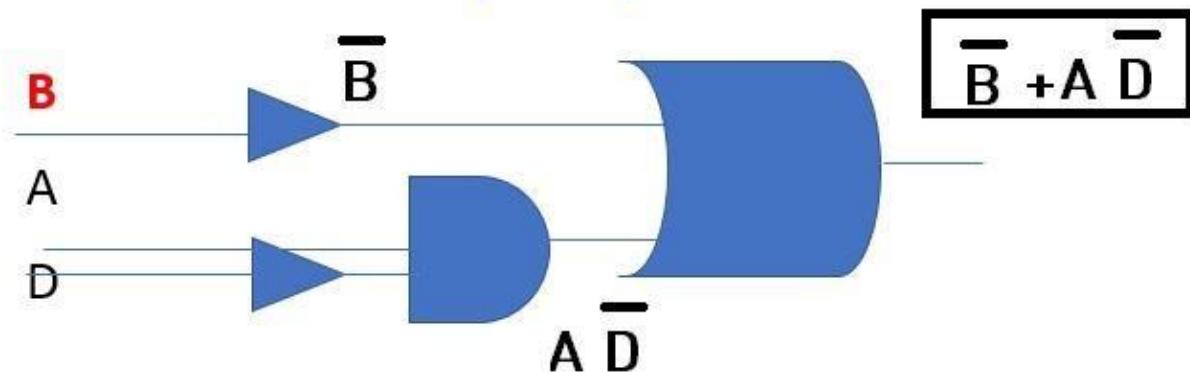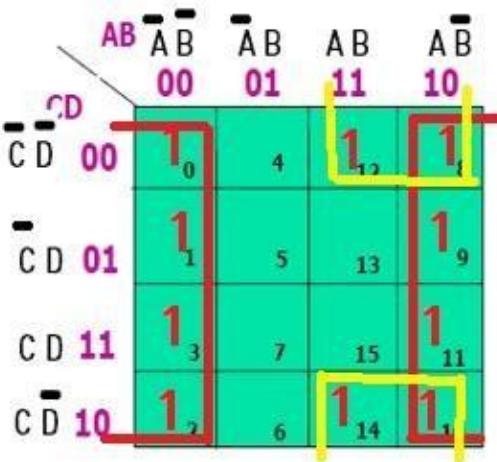
solve using kmap $F = A B C \bar{D} + \bar{B} \bar{C} + \bar{B} D + A B \bar{C} \bar{D} + \bar{B} C$



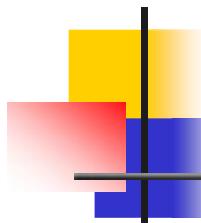


Solve using kmap $Y = A B \bar{C} + A \bar{B} C D + A D + \bar{B} C \bar{D}$

A D + A B \bar{C} + $\bar{B} C \bar{D}$

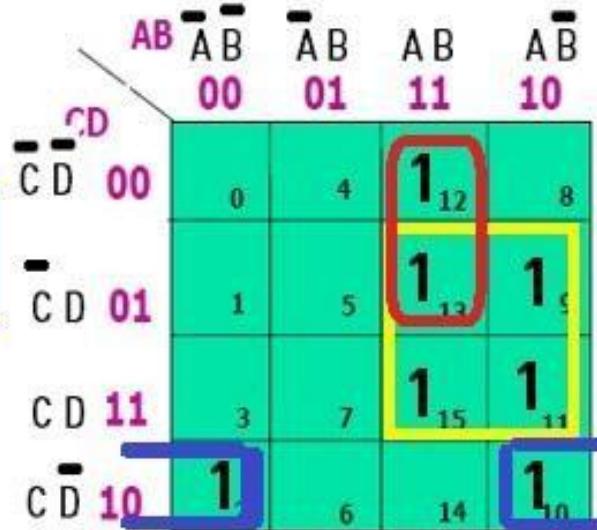


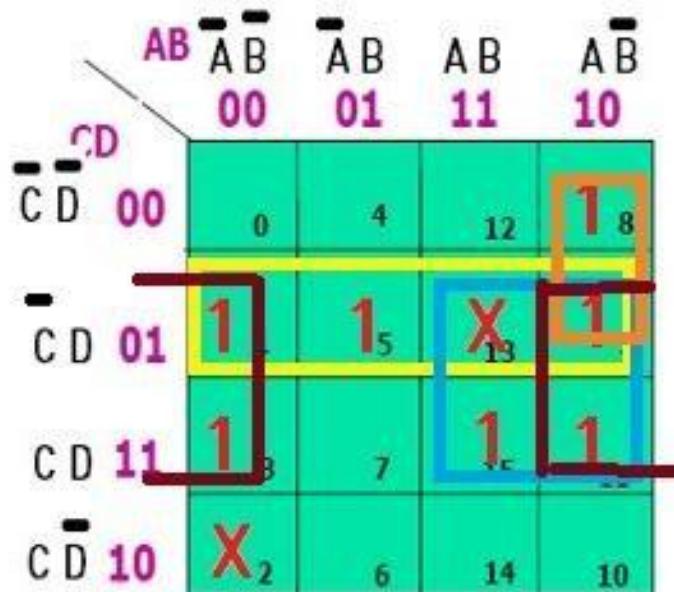Solve using KMAP $F = m[1,3,5,8,9,11,15]. d[2,13]$



$$F = C'D + AD + B'D + AB'C'$$

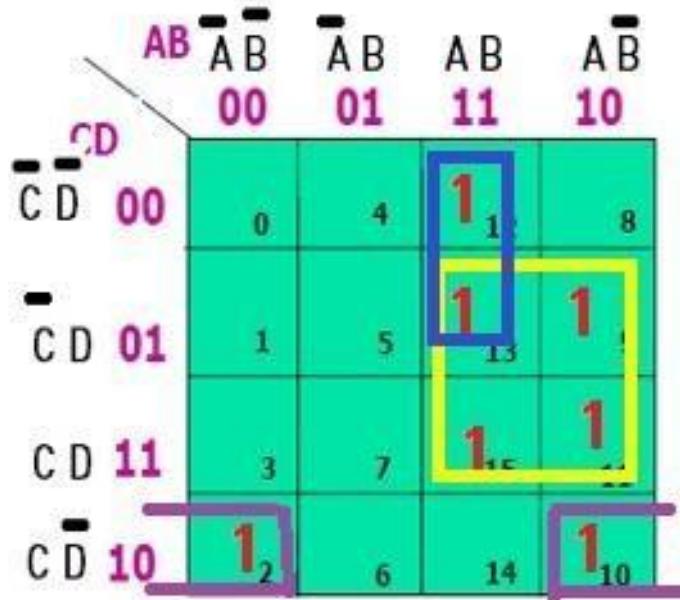Solve using kmap $Y = A B \bar{C} + A \bar{B} C D + A D + \bar{B} C \bar{D}$



$$F = AD + ABC' + B'CD'$$

| | AB | $\bar{A}\bar{B}$ | $\bar{A}B$ | AB | $A\bar{B}$ | |
|------------------|------|------------------|------------|------|------------|----|
| CD | 00 | 01 | 11 | 10 | | |
| $\bar{C}\bar{D}$ | 00 | 01 | 11 | 10 | | |
| 00 | 0 | 4 | 1 | 12 | 1 | 8 |
| 01 | 1 | 5 | 1 | 13 | 1 | 9 |
| 11 | 3 | 7 | 1 | 15 | 1 | 11 |
| 10 | 2 | 6 | 1 | 14 | 1 | 19 |

$$F = \sum(8, 9, 10, 11, 12, 13, 14, 15)$$

$$F = A$$

| | $A\bar{B}\bar{A}\bar{B}$ | $\bar{A}B$ | AB | $A\bar{B}$ |
|------------------|--------------------------|------------|------|------------|
| $C\bar{D}$ | 00 | 01 | 11 | 10 |
| $\bar{C}\bar{D}$ | 0 | 14 | 12 | 18 |
| $\bar{C}D$ | 1 | 15 | 13 | 9 |
| CD | 13 | 9 | 15 | 11 |
| $C\bar{D}$ | 12 | 6 | 14 | 10 |
| | 1 | 2 | 3 | 4 |

$$F = \sum m(2, 3, 4, 5, 8, 9, 14, 15)$$

$$F = \bar{A}\bar{B}C + \bar{A}B\bar{C} + AB\bar{C} + A\bar{B}\bar{C}$$

$$F = A \oplus B \oplus C$$

| | $\bar{A}B$ | $\bar{A}B$ | AB | $A\bar{B}$ | |
|------------------|------------|------------|------|------------|---|
| $\bar{C}D$ | 00 | 01 | 11 | 10 | |
| $\bar{C}\bar{D}$ | 8 | 10 | 4 | 12 | 1 |
| $C\bar{D}$ | 1 | 5 | 13 | 9 | |
| $C\bar{D}$ | 3 | 7 | 15 | 11 | |
| $C\bar{D}$ | 10 | 2 | 6 | 14 | 1 |

$$F = \Sigma(0, 2, 8, 10, 5, 3, 13, 15)$$

$$F = B\bar{D} + \bar{B}\bar{D}$$

① $B\bar{D}$

② $\bar{B}\bar{D}$

| CD | AB | $\bar{A}\bar{B}$ | $\bar{A}B$ | $A\bar{B}$ | AB | $A\bar{B}$ |
|-------------|----|------------------|------------|------------|------|------------|
| CD | 00 | 01 | 11 | 10 | | |
| $\bar{C}D$ | 00 | 01 | 12 | 13 | 14 | 15 |
| C \bar{D} | 1 | 7 | 15 | 11 | | |
| C D | 3 | 5 | 13 | 1 | 9 | 8 |
| $C\bar{D}$ | 2 | 6 | 14 | 10 | 1 | 4 |
| CD | 01 | 11 | 10 | 10 | 00 | 00 |


$$F = A\bar{B}\bar{C} + \bar{A}\bar{B}C + C\bar{D}$$

$$F = A\bar{B} + C\bar{D}$$


① $A\bar{B}$

② $C\bar{D}$

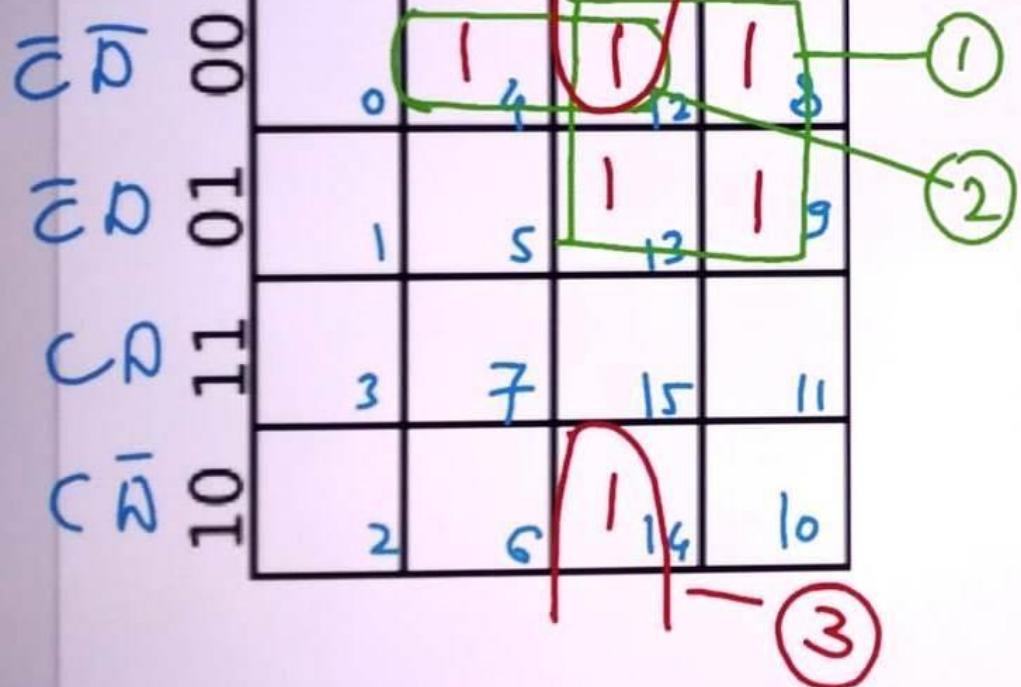
$$\begin{array}{c} \text{AB} \\ \diagdown \quad \diagup \\ \text{CD} \end{array} \quad \begin{array}{c} \bar{A}\bar{B} \\ \bar{A}B \\ AB \\ A\bar{B} \end{array} \quad \begin{array}{c} 00 \\ 01 \\ 11 \\ 10 \end{array} \quad F = \sum m(4, 8, 9, 12, 13, 14)$$


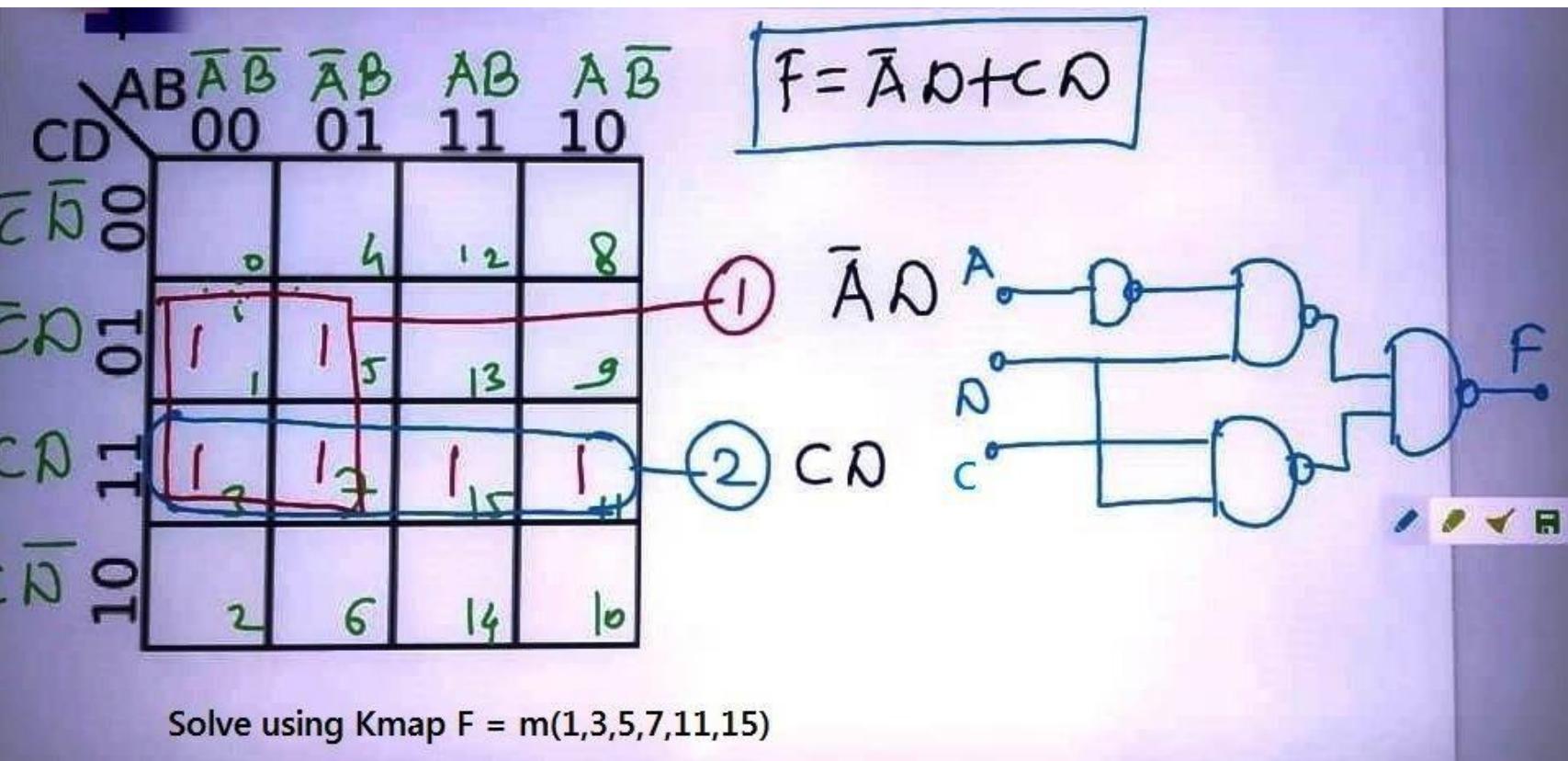
$$F = A\bar{C} + B\bar{C}\bar{D} + A\bar{B}\bar{D}$$




| CD | $A\bar{B}\bar{A}\bar{B}$ | $\bar{A}B$ | AB | $A\bar{B}$ |
|------------------|--------------------------|------------|------|------------|
| $\bar{C}\bar{D}$ | 00 | 01 | 11 | 10 |
| $\bar{C}D$ | 1 | 5 | 12 | 8 |
| $C\bar{D}$ | 1 | 5 | 13 | 9 |
| CD | 3 | 7 | 11 | 10 |
| $C\bar{D}$ | 2 | 6 | 14 | 10 |

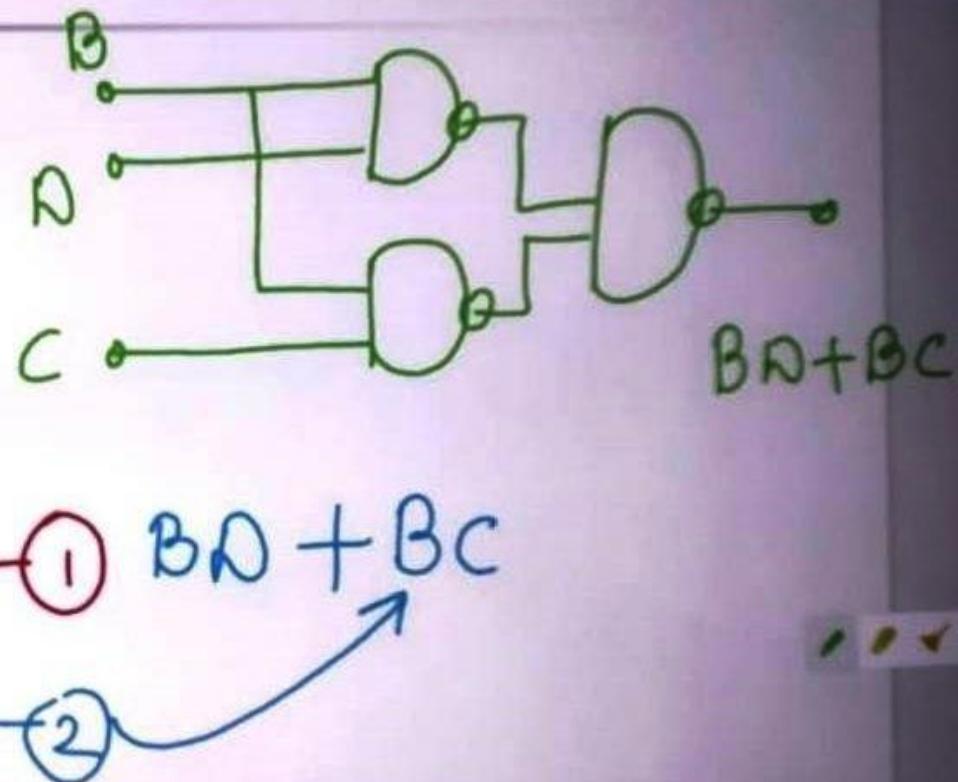


For given logic equation $F = ABC + B\bar{C}D + \bar{A}\bar{B}C$

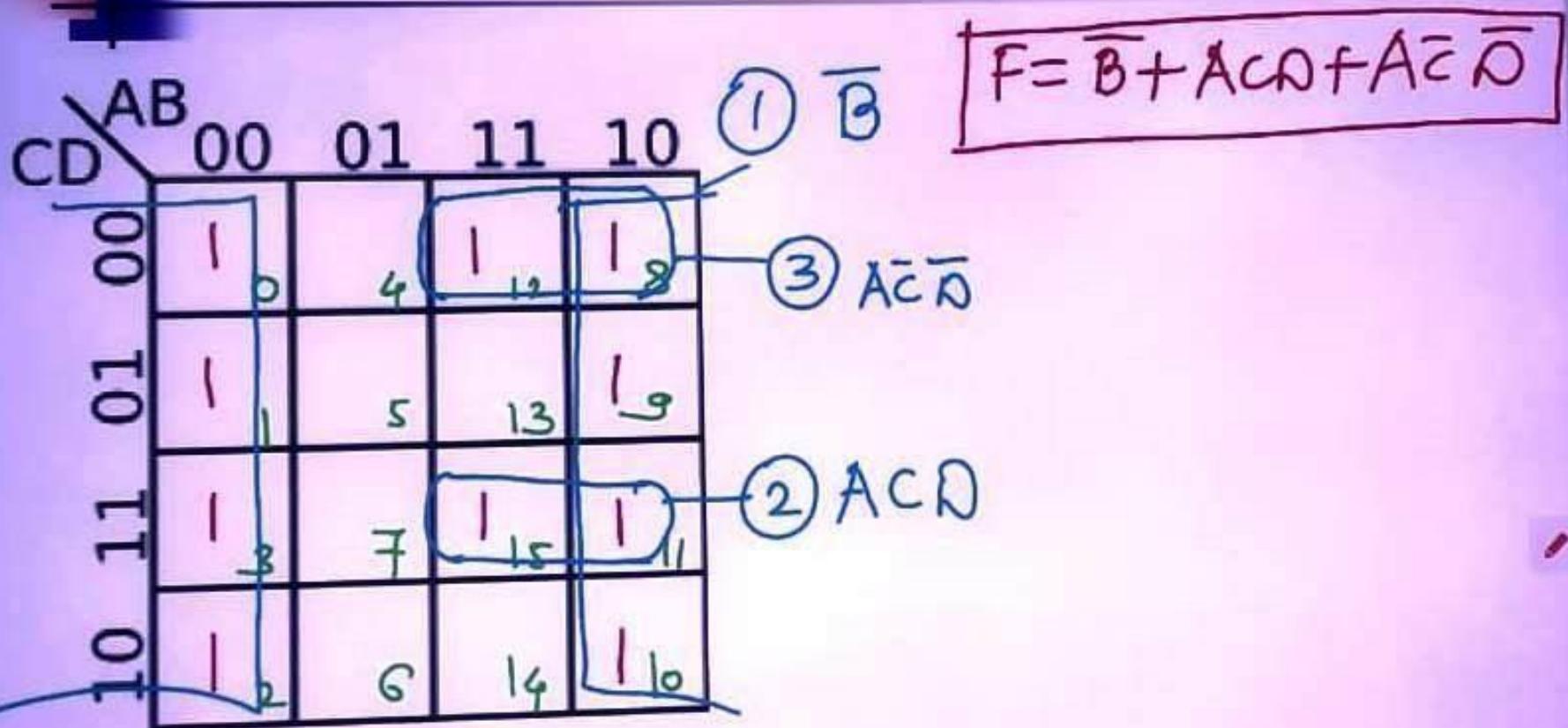For given equation $F = ABC\bar{D} + \bar{B}\bar{C} + \bar{B}D + ABC\bar{D} + \bar{B}C$ simplify using Kmap




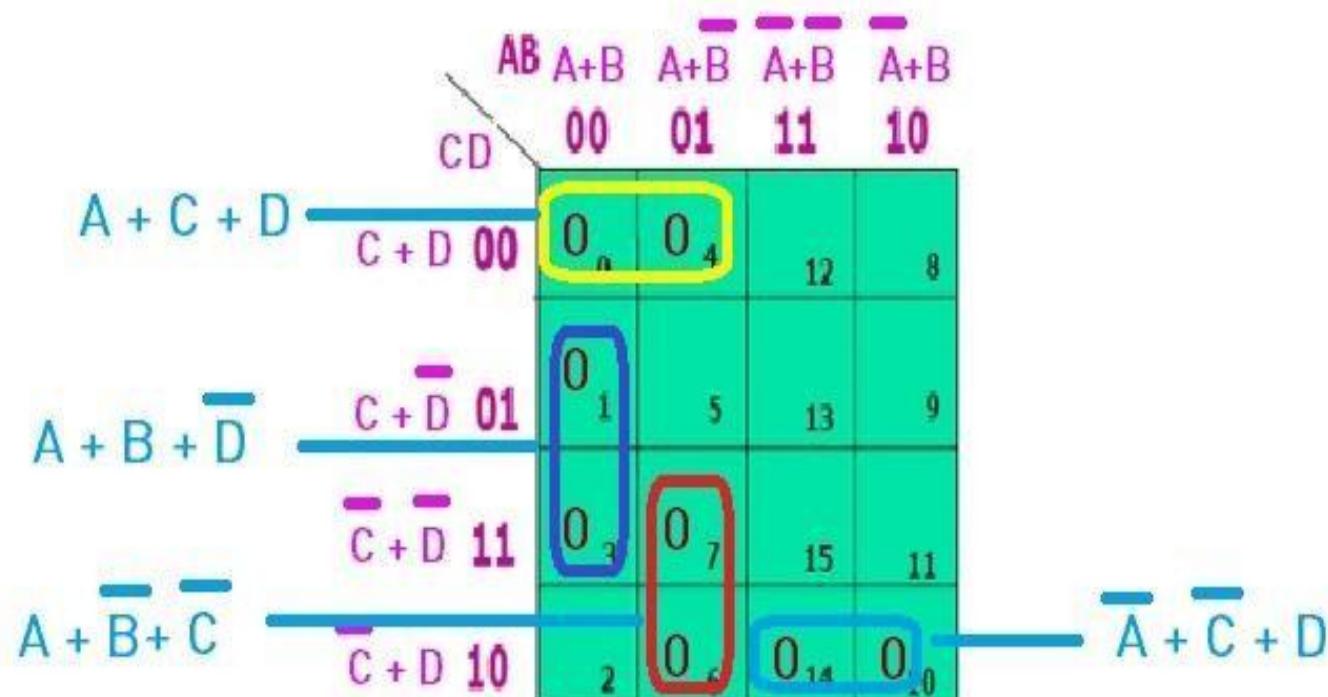solve using kmap $F = M(0,1,3,4,6,7,10,14)$



$$F = (A + C + D) \cdot (A + B + \bar{D}) \cdot (A + \bar{B} + C) \cdot (\bar{A} + \bar{C} + D)$$

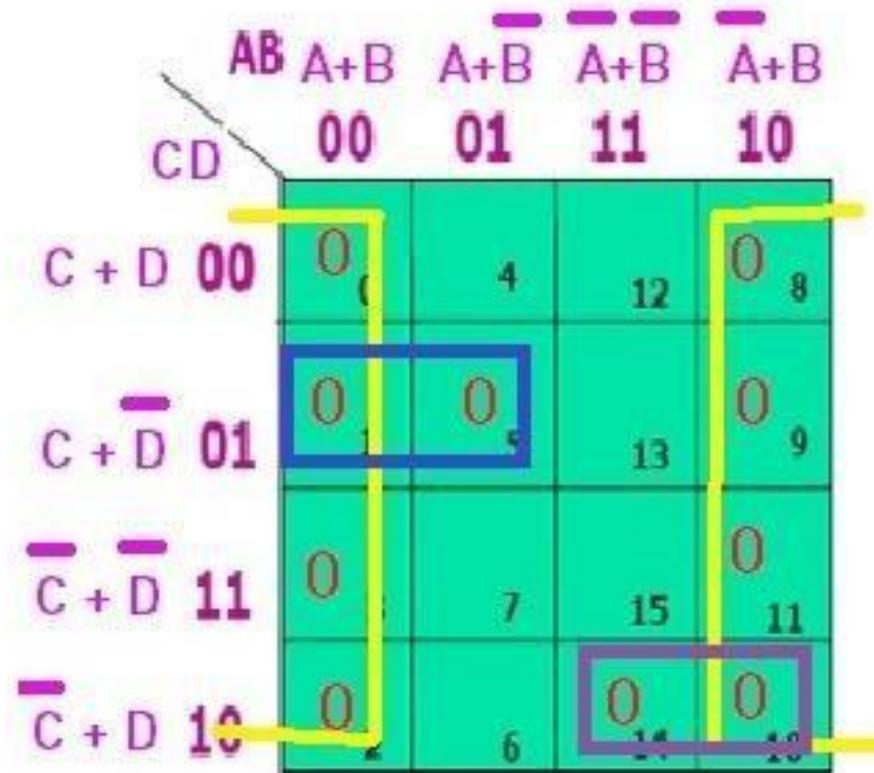
solve using kmap $F = M(0,1,2,3,5,8,9,10,11,14)$



POS
 $A=0$
 $A'=1$

$$F = (B)(A+C+D')(A'+C+D')$$

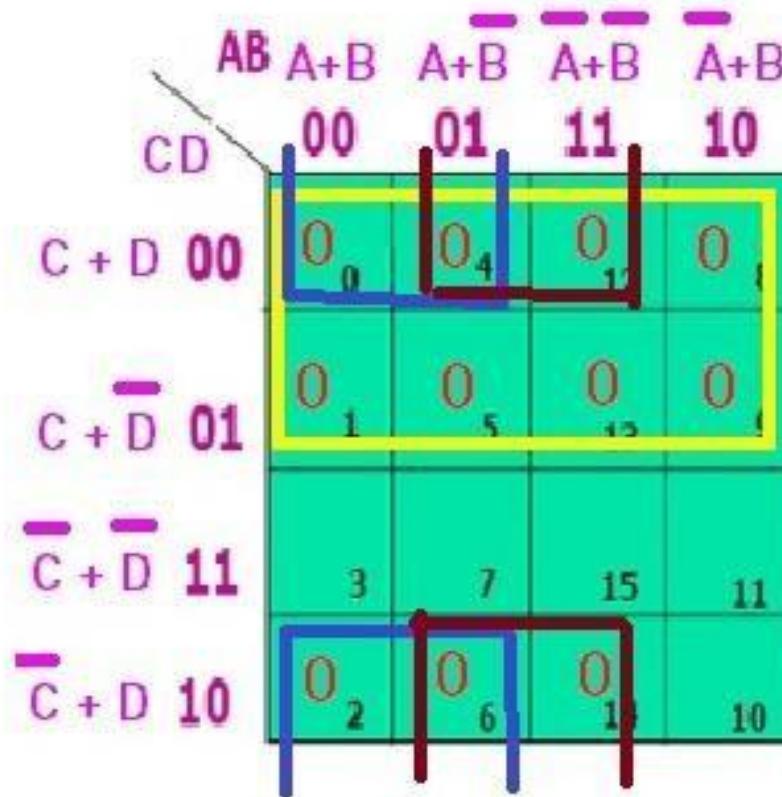solve using kmap $F = M\{0,1,2,4,5,6,8,9,12,13,14\}$



POS
 $A=0$
 $A'=1$

$$F = (C).(A+D).(B'+D)$$

solve using kmap $F = M(0,1,3,4,6,7,10,14)$

| | | AB | A+B | A+B | A+B | A+B |
|---------------|----|----------------|----------------|-----------------|-----|-----|
| | | CD | 00 | 01 | 11 | 10 |
| C + D | 00 | 0 ₀ | 0 ₄ | | 12 | 8 |
| | 01 | 0 ₁ | | 5 | 13 | 9 |
| $\bar{C} + D$ | 11 | 0 ₂ | 0 ₇ | | 15 | 11 |
| | 10 | 2 | 0 ₆ | 0 ₁₀ | | 14 |

$$A+C+D$$

$$A+B+D'$$

$$A+B'+C'$$


$$(A'+C'+D)$$

$$F = (A+C+D)(A+B+D')(A+B'+C')(A'+C'+D)$$

Don't Care condition in KMAP :

1. It is represented by symbol 'X' in kmap
2. It has the value either 0 or 1. We may have to assume the value of it either 0 or 1 as per our convenience


$$F = m(1,3,7,11,15). d(0,2,8,12)$$

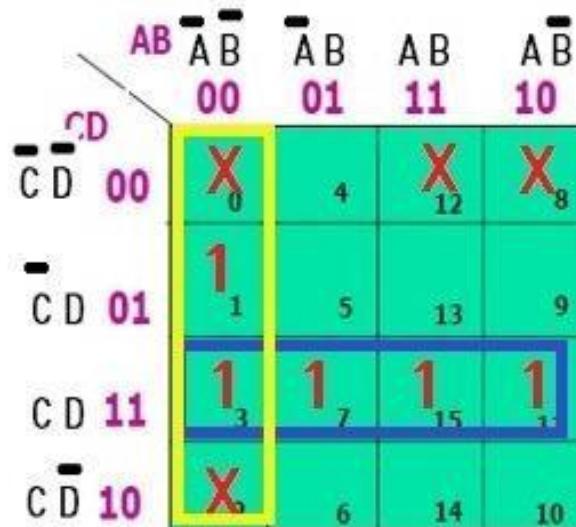


$$F = CD + A'B'$$

Solve the following using KMAP
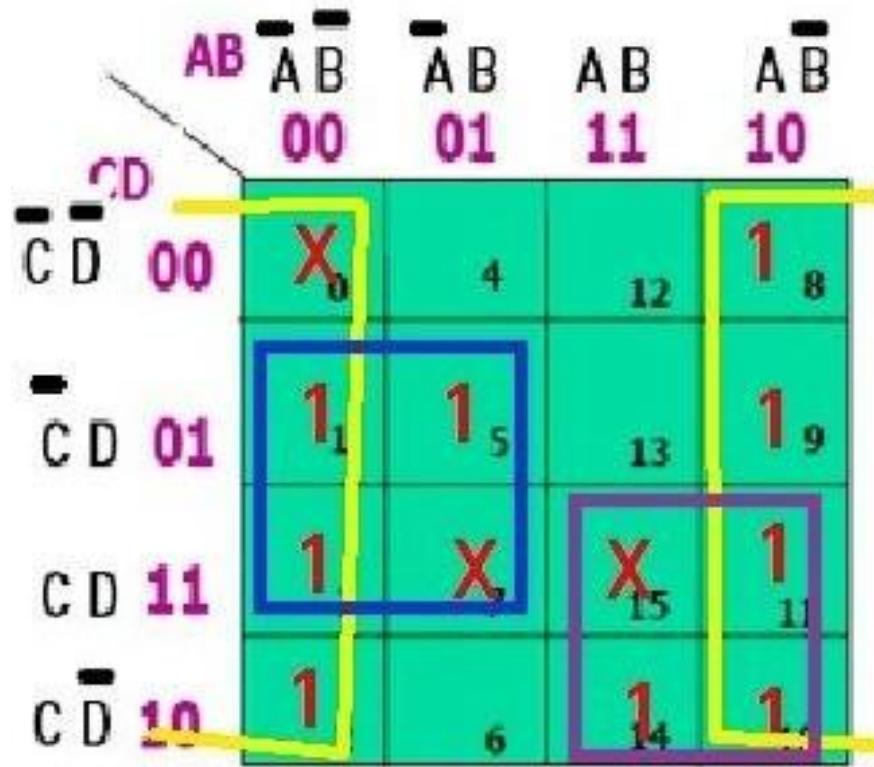
$$F = m(1, 2, 3, 5, 8, 9, 10, 11, 14) \cdot d(0, 7, 15)$$



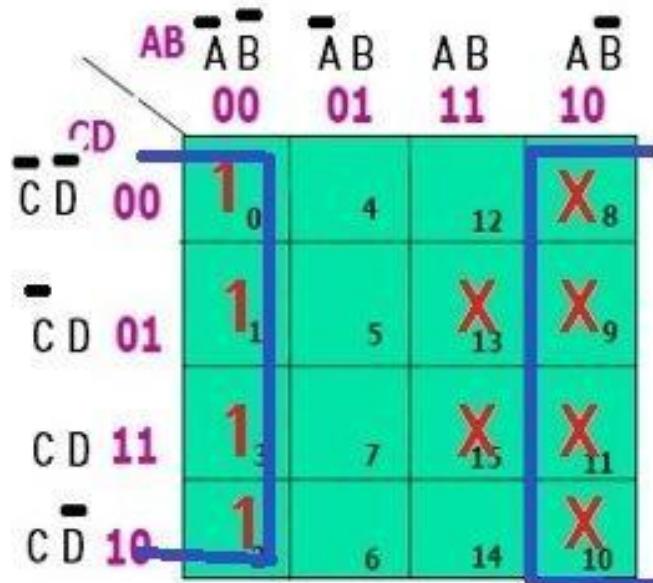Solve using KMAP $F = \{0, 1, 2, 3\}$. $d\{8, 9, 10, 11, 13, 15\}$




$$F = B'$$

Calculate $F(A,B,C,D) = \pi M(4,5,6,7,8,12) \cdot d(1,2,3,11,14)$.

| | | $\bar{A}\bar{B}$ | $A+B$ | $A+\bar{B}$ | $\bar{A}+B$ | $\bar{A}+\bar{B}$ |
|---------------------|------|------------------|----------------|-----------------|-----------------|-------------------|
| | | 00 | 01 | 11 | 10 | 11 |
| $C + D$ | 00 | 0 | 0 ₄ | 0 ₁₂ | 0 ₁₃ | 0 ₁₄ |
| | 01 | X_1 | 0 ₅ | 13 | 9 | |
| $\bar{C} + \bar{D}$ | 11 | X_3 | 0 ₇ | 15 | X_{11} | |
| | 10 | X_2 | 0 ₆ | X_{14} | 10 | |

$$F = (A + B') (A' + C + D)$$

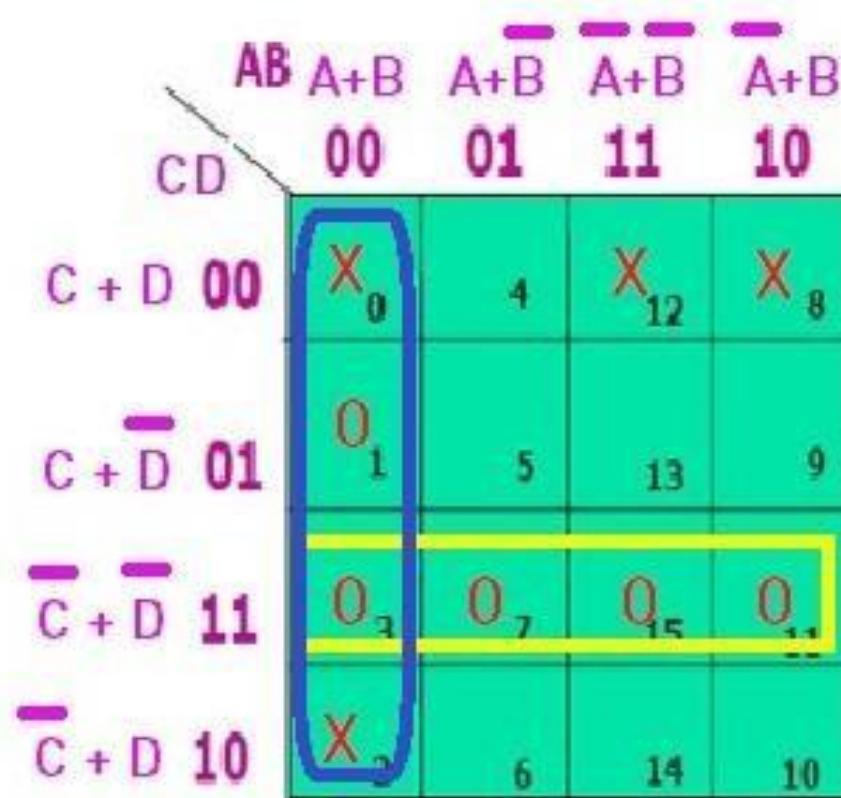solve using kmap $F = M(1,3,7,11,15) \cdot D(0,2,8,12)$




$$F = (C' + D') (A + B)$$

K-map for 5 Variable

| | | \bar{A} | | | |
|------------|----|------------|------------|------|------------|
| | | $\bar{B}C$ | $B\bar{C}$ | BC | $B\bar{C}$ |
| | | 00 | 01 | 11 | 10 |
| $D\bar{E}$ | 00 | 0 | 4 | 12 | 8 |
| | 01 | 1 | 5 | 13 | 9 |
| | 11 | 3 | 7 | 15 | 11 |
| | 10 | 2 | 6 | 14 | 10 |

| | | A | | | |
|------------|----|------------|------------|------|------------|
| | | $\bar{B}C$ | $B\bar{C}$ | BC | $B\bar{C}$ |
| | | 00 | 01 | 11 | 10 |
| $D\bar{E}$ | 00 | 16 | 20 | 28 | 24 |
| | 01 | 17 | 21 | 29 | 25 |
| | 11 | 19 | 23 | 31 | 27 |
| | 10 | 18 | 22 | 30 | 26 |

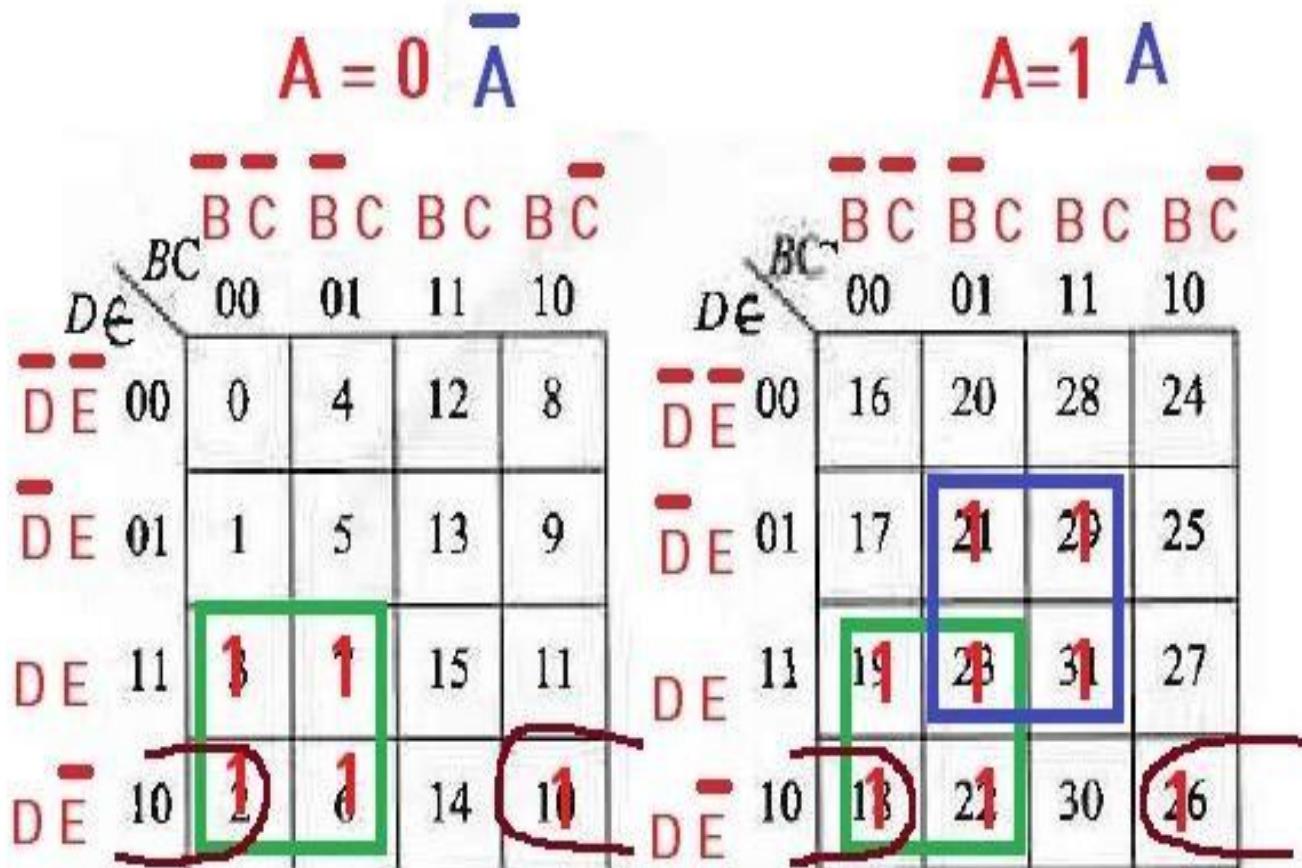Solve using KMAP $F = m(2,3,6,7,10,18,19,21,22,23,26,29,31)$



$$F = A' B' D + A' C' D E' + A B' D + A C E + A C' D E'$$

Solve using Kmap $F = 0, 1, 4, 5, 10, 11, 14, 15, 16, 17, 20, 21, 24, 25, 26, 27$

$A = 0 \quad \bar{A}$

| | | BC | | BC | | BC | | BC | |
|----|--|----|----|----|----|----|--|----|--|
| | | 00 | 01 | 11 | 10 | | | | |
| DE | | 00 | 1 | 1 | 12 | 8 | | | |
| DE | | 01 | 1 | 1 | 13 | 9 | | | |
| DE | | 11 | 3 | 7 | 15 | 11 | | | |
| DE | | 10 | 2 | 6 | 11 | 11 | | | |

$A=1 \quad A$

| | | BC | | BC | | BC | | BC | |
|----|--|----|----|----|----|----|--|----|--|
| | | 00 | 01 | 11 | 10 | | | | |
| DE | | 00 | 1 | 2 | 28 | 24 | | | |
| DE | | 01 | 1 | 2 | 29 | 25 | | | |
| DE | | 11 | 19 | 23 | 31 | 27 | | | |
| DE | | 10 | 18 | 22 | 30 | 26 | | | |

$$F = A'B'D' + A'BD + AB'D' + ABC'$$

$$F = B'D' + A'BD + ABC'$$


$$F(PQRST) = \sum(0, 2, 4, 7, 8, 10, 12, \\ 16, 18, 20, 23, 24, 25, \\ 26, 27, 28)$$

5-variable

$$F(PQRST) = \sum(0, 2, 4, 7, 8, 10, 12, \\ 16, 18, 20, 23, 24, 25, \\ 26, 27, 28)$$


5-variable
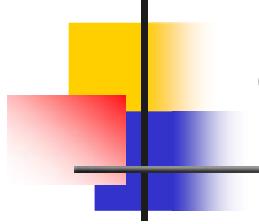
$$F = (S'T') + (R'T') + (Q'RST) + (PQR')$$



Q. Solve using K-map,
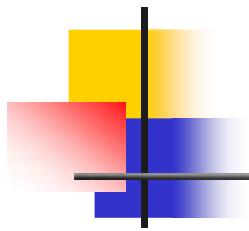
$$F(A,B,C,D,E) = m(0,1,7,9,11,13,15,16,17,23,25,27)$$




Q. Solve using K-map,

$$F(A,B,C,D,E) = m(0,1,7,9,11,13,15,16,17,23,25,27)$$


Answer:
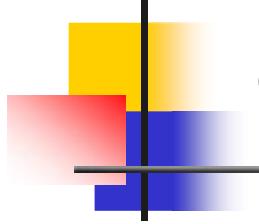
$$\begin{aligned} & B'C'D' + B'CDE + BC'E + A'BE \\ & = B'(C'D' + CDE) + BE(A' + C') \end{aligned}$$



Q. Solve using K-map,
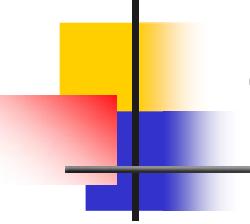
$$F(A,B,C,D,E) = m(0,2,5,7,13,15,18,20,21,23,28,29,31)$$




Q. Solve using K-map,

$$F(A,B,C,D,E) = m(0,2,5,7,13,15,18,20,21,23,28,29,31)$$

Answer:


$$\begin{aligned} & A'B'C'E' + B'C'DE' + CE + ACD' \\ & = B'C'E'(A'+D) + C(E+AD') \end{aligned}$$

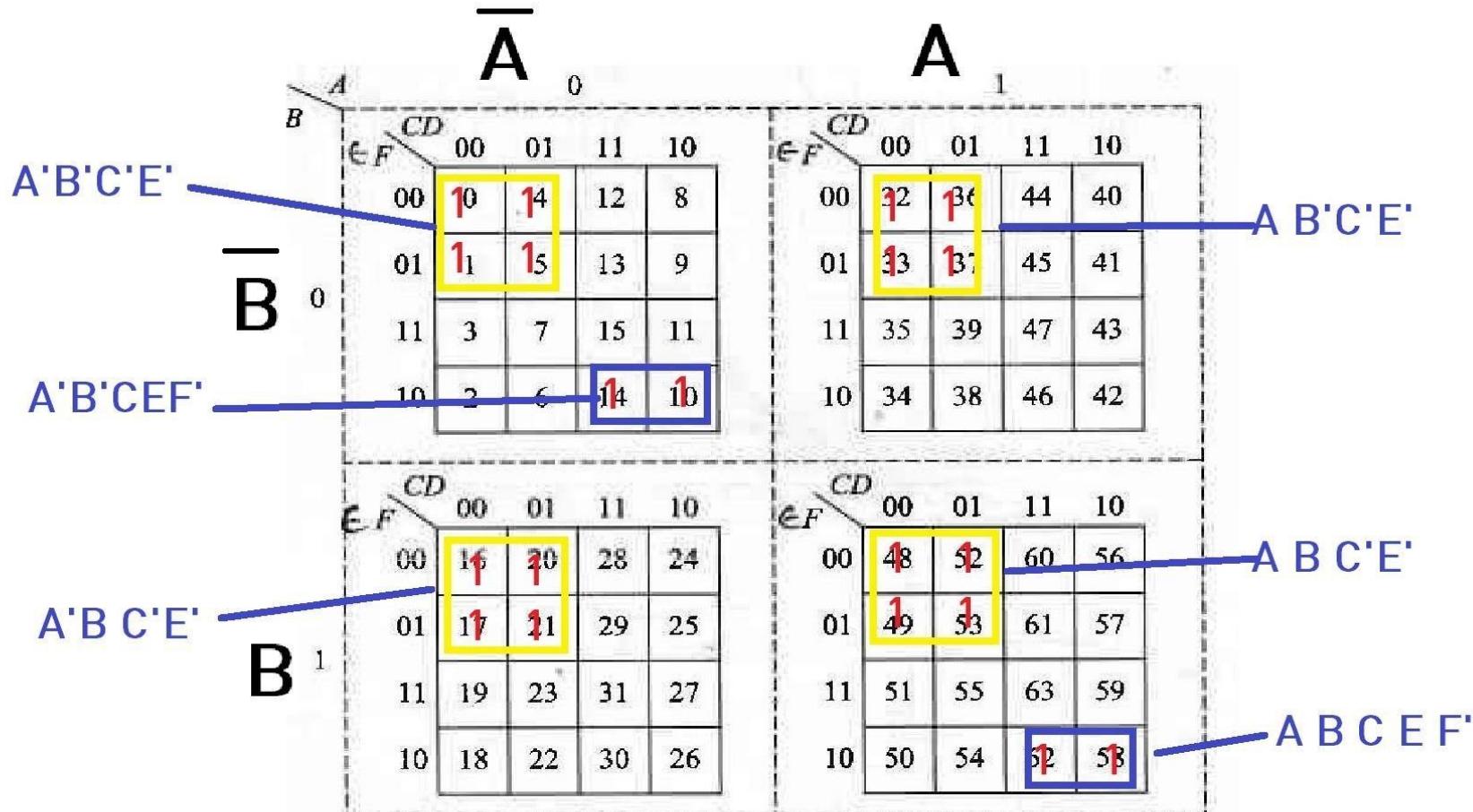Solve using KMAP $F = m(0,1,4,5,10,14,16,17,20,21,32,33,36,37,48,49,52,53,58,62)$



$$F = C'E' + (A \text{ XNOR } B)CEF$$

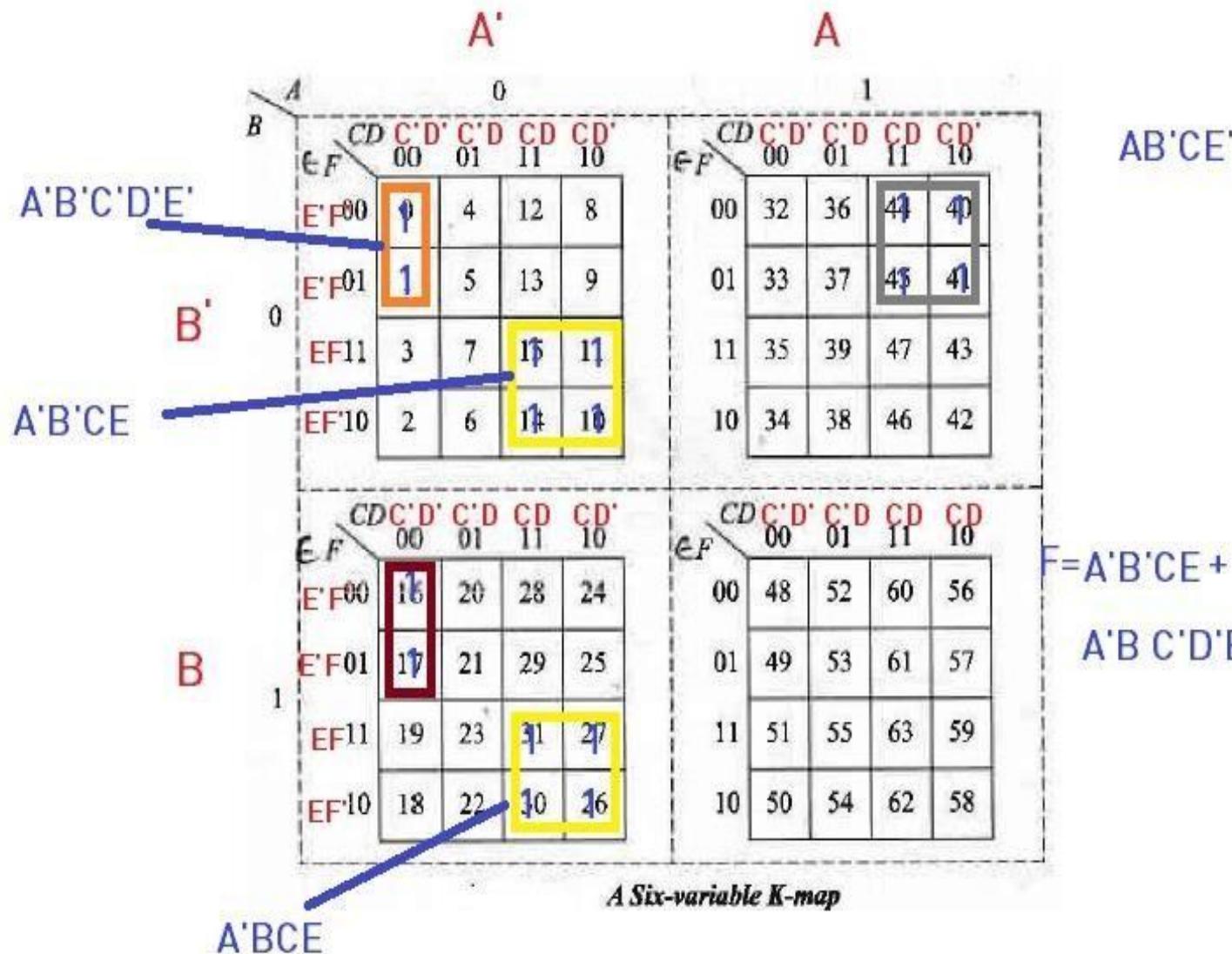Solve the function using kmap $F = m(0,1,10,11,14,15,16,17,26,27,30,31,40,41,44,45)$



$$F = A'B'CE + A'B'C'D'E' + A'BCE + A'B'C'D'E' + AB'CE'$$

•

Q. Solve using Quine-McClusky Tabulation Method,

$$F(A,B,C,D) = m(0,1,3,7,8,9,11,15)$$

T-1.

| Minterms | Binary | | | |
|----------|--------|---|---|---|
| | A | B | C | D |
| 0 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 0 | 1 |
| 3 | 0 | 0 | 1 | 1 |
| 7 | 0 | 1 | 1 | 1 |
| 8 | 1 | 0 | 0 | 0 |
| 9 | 1 | 0 | 0 | 1 |
| 11 | 1 | 0 | 1 | 1 |
| 15 | 1 | 1 | 1 | 1 |

T-2

| Group | Minterms | | | Variables. |
|-------|----------|---|---|------------|
| | A | B | C | D |
| 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 1 |
| 2 | 3 | 0 | 0 | 1 |
| 3 | 5 | 1 | 0 | 0 |
| 4 | 7 | 0 | 1 | 1 |
| | 11 | 1 | 0 | 1 |
| | 15 | 1 | 1 | 1 |

T-3

| Group | Minterms | | | Variables. |
|-------|----------|----|---|------------|
| | A | B | C | D |
| 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 2 | 1 | 3 | 0 | 0 |
| 3 | 1 | 5 | 0 | 0 |
| 4 | 8 | 9 | 1 | 0 |
| 5 | 9 | 7 | 0 | 1 |
| 6 | 9 | 11 | 0 | 1 |
| 7 | 9 | 11 | 1 | 0 |
| 8 | 7 | 15 | 1 | 1 |
| 9 | 11 | 15 | 1 | 1 |

T-4.

| Group | Minterms | | | Variables |
|-------|-----------|---|----|-----------|
| | A | B | C | D |
| 0 | 0,1,8,9 | — | 0 | 0 |
| | 0,8,1,9 | — | 0 | 0 |
| 1 | 1,3,9,11 | — | 0 | —1 |
| | 1,9,3,11 | — | 0 | —1 |
| 2 | 3,7,11,15 | — | —1 | 1 |
| | 3,11,7,15 | — | —1 | 1 |

Prime-Implicants

| P.I. | Decimal | Minterms. |
|------------------|-----------|--------------|
| $\bar{B}\bar{C}$ | 0,1,8,9 | x x x x |
| $\bar{B}D$ | 1,3,9,11 | x x x x |
| CD | 3,7,11,15 | x x x x |

$$Y = \bar{B}\bar{C} + CD$$

MC-CLUSKEY METHOD (TABULAR FORM)

$$f = (a, b, c, d) = \Sigma (0, 5, 8, 9, 10, 11, 14, 15)$$

0 = 0000
 5 = 0101
 8 = 1000
 9 = 1001
 10 = 1010
 11 = 1011
 14 = 1110
 15 = 1111

| STEP = 1 | | | | | |
|----------|---------|----------|---|---|---|
| Group | minterm | variable | | | |
| | | A | B | C | D |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 1 | 8 | 1 | 0 | 0 | 0 |
| 2 | 5 | 0 | 1 | 0 | 1 |
| | 9 | 1 | 0 | 0 | 1 |
| | 10 | 1 | 0 | 1 | 0 |
| 3 | 11 | 1 | 0 | 1 | 1 |
| | 14 | 1 | 1 | 1 | 0 |
| 4 | 15 | 1 | 1 | 1 | 1 |

| STEP = 3 | | | | |
|--------------|-----------------------|----------|----------|------------|
| Group | matched pair | variable | | |
| | | A | B | C |
| 0 | 8, 9, 10, 11 | 1 | 0 | - - |
| A' B' | 8, 10, 9, 11 | 1 | 0 | - - |
| 1 | 10, 11, 14, 15 | 1 | - | 1 - |
| A C | 10, 14, 11, 15 | 1 | - | 1 - |
| | 0, 8 | - | 0 0 0 | |
| | 5 | 0 1 0 1 | | |

| STEP = 2 | | variable |
|----------|--------------|----------|
| Group | matched pair | A B C D |
| 0 | 0, 8 | - 0 0 0 |
| 1 | 8, 9 | 1 0 0 - |
| | 8, 10 | 1 0 - 0 |
| 2 | 9, 11 | 1 0 - 1 |
| | 10, 11 | 1 0 1 - |
| | 10, 14 | 1 - 1 0 |
| 3 | 11, 15 | 1 - 1 1 |
| | 14, 15 | 1 1 1 - |

| P.I | 0 | 5 | 8 | 9 | 10 | 11 | 14 | 15 |
|-------------|---|---|---|---|----|----|----|----|
| 8,9,10,11 | | | X | X | X | X | | |
| 10,11,14,15 | | | | | X | X | X | X |
| 0, 8 | X | | | X | | | | |
| 5 | | X | | | | | | |

$$= A' B' + A C + B' C'D' + A'B C'D$$

$$1) F(ABCD) = \pi m(0, 2, 3, 6, 7, 8, 9, 12, 13)$$

$$2) F(ABCD) = \pi m(0, 2, 4, 5, 7, 8, 9, 10, 13, 14, 15)$$

$$3) F(ABC'DE) = \pi m(2, 3, 5, 8, 9, 10, 11, 17, 18, 19, 21, 24, 25, 26, 27, 29)$$

$$4) F(ABC'D) = \pi m(0, 5, 7, 8, 9, 10, 11, 13)$$

~~$$5) F(A'BCD) = \pi m(1, 2, 4, 5, 7, 8, 10, 11, 13, 14)$$~~

$$6) F(AB'C'D) = \pi m(4, 6, 8, 9, 10, 12, 13, 14) + d(0, 2, 5)$$

7) Find expression in POS form for given function

$$F(AB'CD) = \sum m(0, 2, 3, 4, 7, 9, 10, 12, 14, 15)$$

$$8) F(ABCD) = \Sigma m(1, 4, 6, 8, 11, 13, 14)$$

Find expression in POS form for above function.

$$9) F(ABCD) = \Sigma m(0, 4, 6, 7, 10, 12, 14) + d(2, 13)$$

Find expression in POS form.

10) Solve using k-map

$$Y = ABC\bar{D} + \bar{B}\bar{C} + \bar{B}D + AB\bar{C}\bar{D} + \bar{B}C$$

11) obtain expression in SOP form

$$a) F_1(ABCD) = \Pi M(2, 7, 8, 9, 10, 12)$$

$$b) F_2(WXY_2) = \Sigma m(1, 3, 7, 11, 15) + d(0, 2, 5)$$

$$12) F(ABCD) = \Sigma m(2, 3, 4, 6, 10, 11) + d(0, 13, 15)$$

13) Simplify using k-map & implement using NAND gate only.

$$F = ABC + \bar{B}\bar{C}D + \bar{A}BC$$

$$14) F = \Sigma m(0, 2, 8, 9, 10, 12, 13, 14)$$

$$15) F = \Pi M(1, 2, 3, 5, 8, 9, 10, 11, 14) + d(0, 7, 15)$$